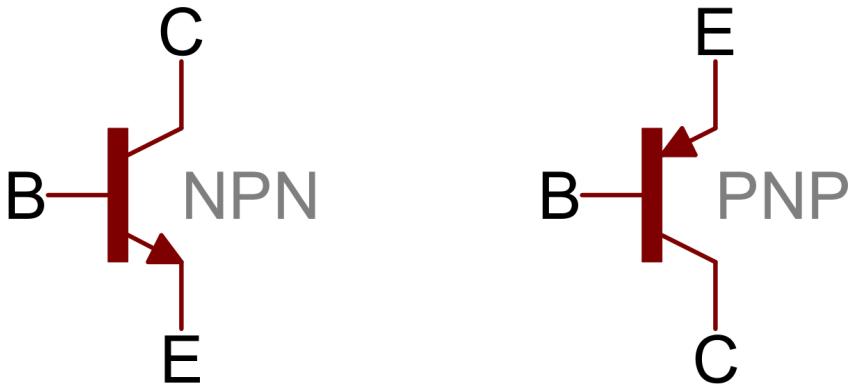



Bipolar Junction Transistor (BJT)

B: Base, C: Collector, E: Emitter

We'll work with NPN transistors for now. PNP are similar, but are kind of like the inverse to NPN

A quick summary of BJTs:

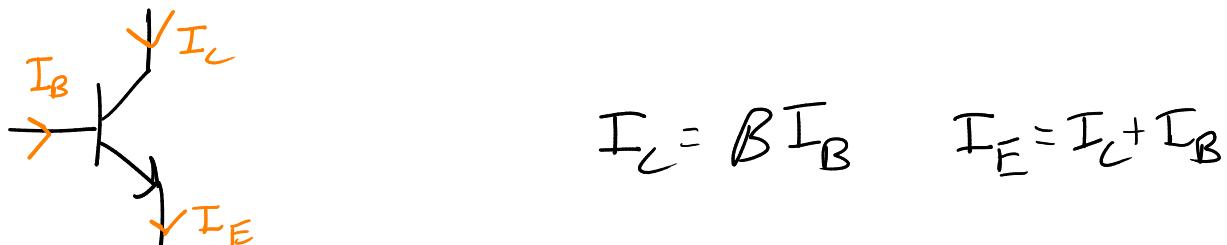They act like current-controlled current sources (CCCS). Here the base is the control, and the collector/emitter are the output. Ignoring non-idealities, the current into the collector is proportional to the current into the base. Both flow out of the emitter.



This isn't quite enough info to build our model. Let's look at the device equation for a BJT:

$$I_C = I_S (e^{\frac{V_{BE}}{V_T}} - 1) \approx I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

This is a good approximation for any reasonable  $V_{BE}$  ( $V_{BE} > 0.1$  V)

$I_C$ : collector current

$V_{BE}$ : Base-emitter voltage

$I_S$ : saturation current, a constant that is dependent on the BJT's physical construction

$V_T$ : Thermal voltage, a constant that equals 26mV at room temperature

It's a nonlinear equation...

Pretty annoying to work with and not terribly intuitive

## Crash course in small-signal analysis: let's pretend it's linear

So our device is nonlinear, but what if our input signal is small? Maybe we can pretend it's linear? We can, and this is called small signal analysis. The technique is very reminiscent of other techniques to approximate a function as easier to work with functions, like Taylor polynomials

The idea here is to split our signal into a DC part and an AC part, then analyze them separately.


$$V_{in} = \underbrace{V_{IN}}_{\substack{\text{total} \\ \text{signal}}} + \underbrace{v_{in}}_{\substack{\text{DC} \\ \text{AC}}}$$

$$V_{out} = \underbrace{V_{OUT}}_{\substack{\text{total} \\ \text{signal}}} + \underbrace{v_{out}}_{\substack{\text{DC} \\ \text{AC}}}$$

And since we are linearizing for the small signal (AC) part,  $v_{out}$  and  $v_{in}$  are proportional.

Small signal:  $v_{out} = \underbrace{A_v}_{\substack{\text{gain}}} v_{in}$

Let's figure out how to do this:

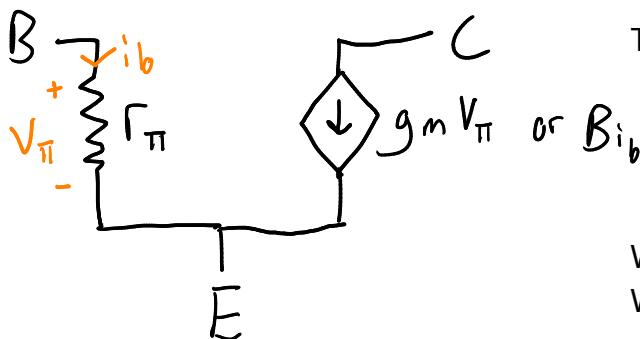

This is the model we'll use. (A simplified hybrid pi model)

We need to figure out what  $g_m$  and  $r_\pi$  are. We will use the equation for  $I_c$  from earlier.

$$g_m = \frac{\text{collector current}}{\text{base emitter voltage}} = \frac{\partial I_c}{\partial V_{BE}} = \frac{I_s}{V_T} e^{\frac{V_{BE}}{V_T}} = \frac{I_c}{V_T}$$

$$r_\pi = \frac{\text{base emitter voltage}}{\text{base current}} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\partial V_{BE}}{\partial I_c} \cdot \beta = \frac{V_T}{I_c} = \frac{\beta}{g_m}$$

The big conclusions:


$$g_m = \frac{I_c}{V_T} \quad r_\pi = \frac{\beta}{g_m}$$

Note: We take the derivatives in this derivation because we are interested in the small-signal parts. i.e. we are only interested effect of the perturbations on top of the DC voltage (or bias)

Here,  $I_c$  is the large signal (DC) current through the collector
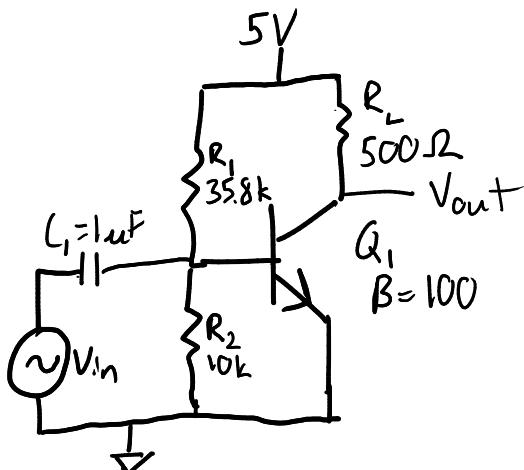
## An example: Common Emitter Amplifier

Let's figure out the rest of this process as we work through an example




Our goal is to calculate the gain of this common-emitter amp. We will assume  $V_{BE} = 0.7V$ , which is often a safe assumption that is guaranteed by the device properties of the BJT.


Here  $C_1$  provides DC blocking, so that we can couple our AC signal into the amplifier while  $R_1$  and  $R_2$  set the bias
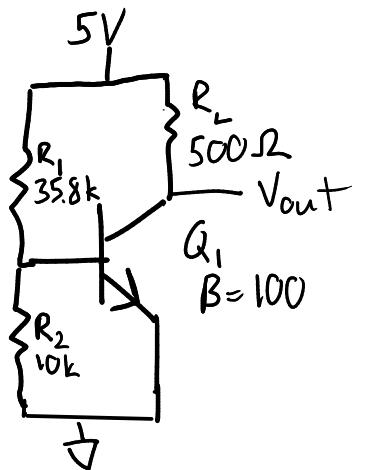
### Step 1: Figure out the DC bias of the amplifier

We can ignore  $V_{in}$ , since that is only an AC signal



Thevenize  
 $R_{th} = R_1 + R_2$

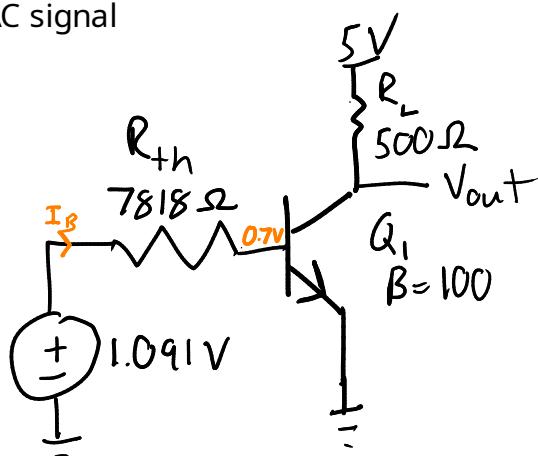


Now, using the assumption that  $V_{BE}=0.7V$

$$I_B = \frac{1.091V - 0.7V}{7818\Omega} = 50\mu A$$

$$\Rightarrow I_C = \beta I_B = 5mA$$

Reminder: Thevenin of a voltage divider

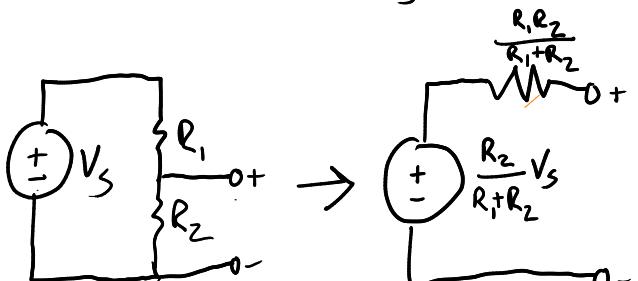

Yay! We've found the bias current! Now we can calculate the small signal parameters. Also, we observe that the output is at 2.5 V. This means we are operating in a region where our assumptions are valid.

**Key Takeaway:** By changing the ratio  $R_1$  and  $R_2$ , we can control the bias current


### Step 2: Calculate small signal parameters

$$g_m = \frac{I_C}{V_T} = 192\text{ mS}$$

$$r_{\pi} = \frac{B}{g_m} = 520\Omega$$
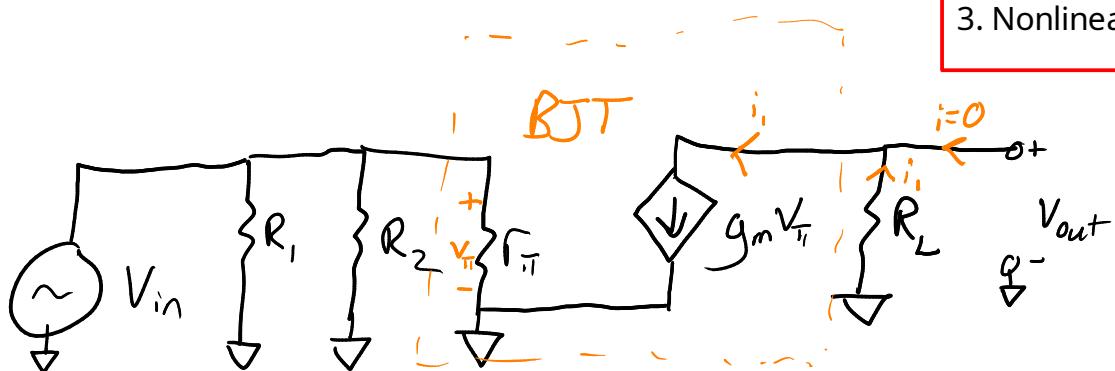
### Step 3: Draw out the small signal model

- Rules for small signal models:
- 1. DC voltage sources become ground
- 2. Large capacitors can go to shorts
- 3. Nonlinear devices get linearized



We do these things because we don't care about the DC portion. Only the small signal, AC portion.

#### Step 4: Solve out to get the gain

Note:  $V_{II} = V_{in} \Rightarrow i_t = g_m V_{in}$

$$V_{out} = -i_1 R_L = -g_m R_L V_{in}$$

$$\text{Gain: } A_v = \frac{V_{\text{out}}}{V_{\text{in}}}$$

$$A_v = -g_m R_L = -96$$

A couple takeaways:

Our gain is increased by  $R_L$

However, increasing  $R_L$  also decreases the DC voltage at the output.

It turns out, that if you fix the output voltage, your gain is purely a function of the supply voltage. So, a good way to think about designing these is to choose some collector current (1-10mA is a decent range for discrete transistors), then choose the other parameters to get your desired DC bias point.