
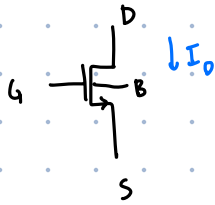


I. MOSFET Overview (Large-Signal)

N-Channel MOSFET (NMOS)

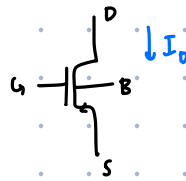


P-Channel MOSFET (PMOS)



D: Drain
G: Gate
S: Source
B: Bulk

Operating Region	NMOS	PMOS
Cutoff	$V_{GS} < V_{TH}$	$V_{SG} < V_{TH} $
Triode	$V_{GS} > V_{TH}$ $V_{DS} < V_{GS} - V_{TH}$	$V_{SG} > V_{TH} $ $V_{SD} < V_{SG} - V_{TH} $
Saturation	$V_{GS} > V_{TH}$ $V_{DS} > V_{GS} - V_{TH}$	$V_{SG} > V_{TH} $ $V_{SD} > V_{SG} - V_{TH} $

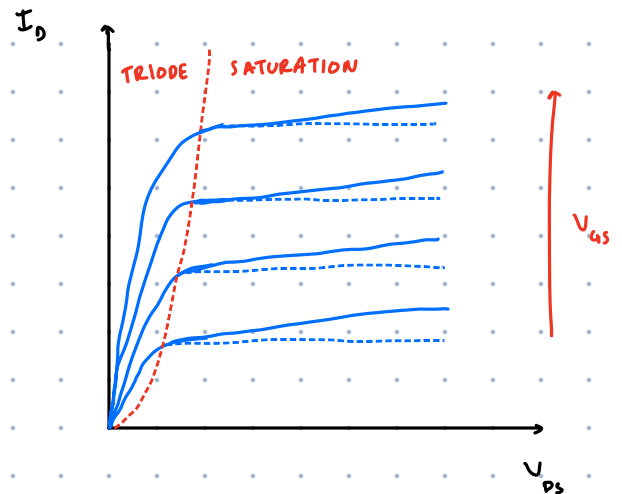

Cutoff: device is OFF

$$I_D = 0$$

Triode: device is ON, linear region (resistor)

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right] (1 + \lambda V_{DS})^*$$

Saturation: device is ON, amplification region (voltage-controlled current source)

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})^*$$

* These equations are for N-channel devices, which we will use for the rest of the recitation. P-channel devices behave analogously (but inversely).

Parameter Description:

μ_n - electron mobility

C_{ox} - oxide capacitance/unit area

W - width of inversion channel

L - length of inversion channel

λ - channel length modulation

• effective channel length decreases as V_{DS} increases

} k_n

II: Small-Signal Model

As we can see, the MOSFET is a non-linear device. This makes circuit analysis hard.

We can linearize our MOSFET by biasing it at a DC operating point to ensure saturation, and look at how small changes in input-voltage (AC) affect the output.


From Rec 3:
$$\left. \begin{array}{l} V_{in} = V_{IN} + v_{in} \\ V_{out} = V_{OUT} + v_{out} \end{array} \right\} v_{out} = A_v v_{in}$$

$$\underbrace{V_{in}}_{\text{total}} = \underbrace{V_{IN}}_{\text{DC}} + \underbrace{v_{in}}_{\text{AC}}$$

$$\underbrace{V_{out}}_{\text{total}} = \underbrace{V_{OUT}}_{\text{DC}} + \underbrace{v_{out}}_{\text{AC}}$$

gain

Simplified Small-Signal Model:

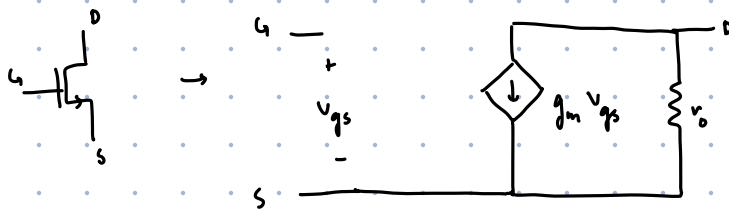

$$g_m = \frac{\partial I_D}{\partial V_{gs}}$$

$$r_o = \frac{\partial V_{DS}}{\partial I_D}$$

For an NMOS in saturation:



$$g_m = \frac{\partial I_D}{\partial V_{gs}} = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th}) = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2 I_D}{V_{gs} - V_{th}}$$

$$r_o = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\lambda I_D}$$

Using our small-signal model, we can apply KCL/KVL to compute gain.

III. MOSFET Amplifiers

Common-Source

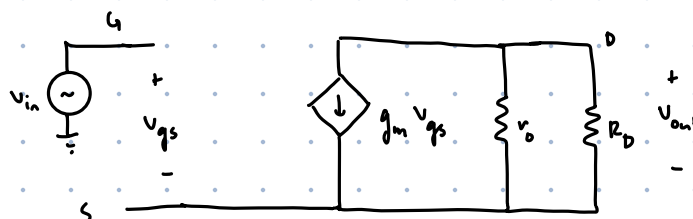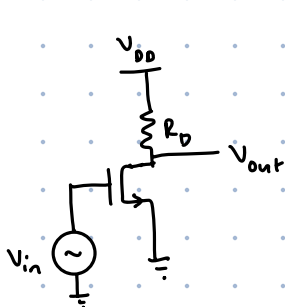



· high input resistance

$$v_{in} = v_{gs}$$

$$v_{out} = -g_m v_{gs} (r_o \parallel R_D)$$

$$a_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R_D)$$

Common - Gate

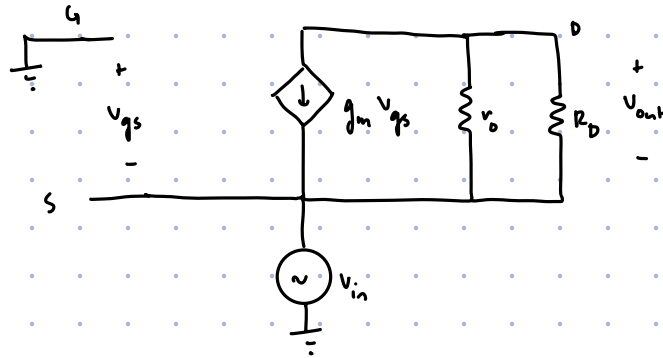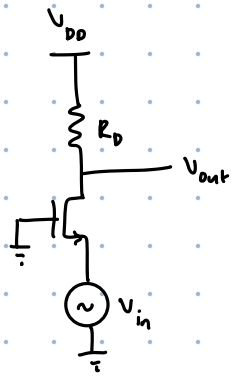



$$V_{in} = -V_{gs}$$

$$V_{out} = -g_m V_{gs} (r_o \parallel R_D)$$

$$a_v = \frac{V_{out}}{V_{in}} = g_m (r_o \parallel R_D)$$

· low input resistance

Common - Drain

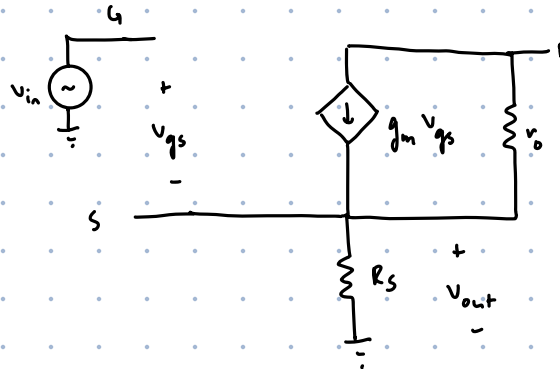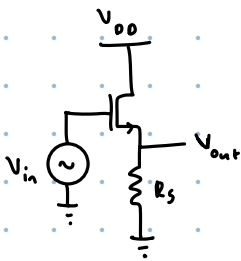

$$V_{in} = V_{gs} + V_{out} \rightarrow V_{gs} = V_{in} - V_{out}$$

$$V_{out} = g_m V_{gs} R_S$$

$$= g_m (V_{in} - V_{out}) R_S$$

$$V_{out} = g_m V_{in} R_S - g_m V_{out} R_S$$

$$V_{out} (1 + g_m R_S) = g_m V_{in} R_S$$

$$a_v = \frac{V_{out}}{V_{in}} = \frac{g_m R_S}{1 + g_m R_S}$$

· high input resistance
· low output resistance