

Recitation 7: Linear Regulator + Switching Regulator


I. Voltage Regulators

- many electronic components require a stable DC voltage
- regulators maintain a constant output voltage despite variations in input voltage and load current
- use feedback / control to correct deviations

	Linear Regulators	Switching Regulators
Control	Variable Resistance	Duty-cycle control
Loss	Heat Dissipation through resistor	Parasitics + Internal resistances of components
Efficiency	Low	High
Conversion Type	Step-Down	Step-Down, Step-Up
Regulation Mechanism	Reference and Feedback	Duty-cycle and energy-balance


II. Linear Regulators

Block Diagram:

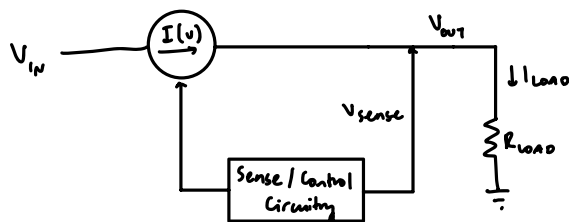

- control circuitry monitors the output voltage + adjusts the current source

LDO Schematic:

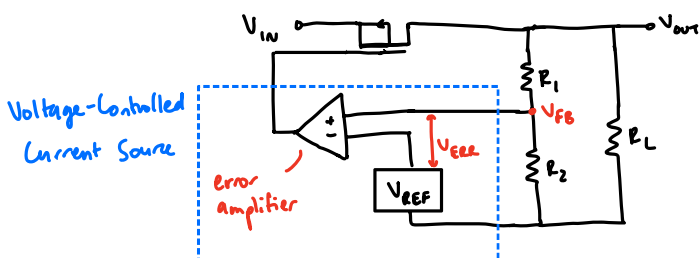

$$V_{EA} = A_{EA} \cdot V_{ERR}$$

• At Regulation:

$$V_{FB} = V_{REF} = \frac{R_2}{R_1 + R_2} V_{OUT}$$

• V_{OUT} too low

$$\begin{aligned} & V_{OUT} \downarrow \\ & \hookrightarrow V_{REF} > V_o \\ & \hookrightarrow V_{ERR} > 0 \\ & \hookrightarrow V_{EA} \uparrow \rightarrow \text{device conduction increases} \\ & \hookrightarrow V_o \uparrow \end{aligned}$$

V_{OUT} too high

$$\begin{aligned} & V_{OUT} \uparrow \\ & \hookrightarrow V_{REF} < V_o \\ & \hookrightarrow V_{ERR} < 0 \\ & \hookrightarrow V_{EA} \downarrow \rightarrow \text{device conduction decreases} \\ & \hookrightarrow V_o \downarrow \end{aligned}$$

• Dropout Voltage: Lowest differential voltage at which the circuit can regulate

$$V_{dropout} = I_o R_{DS(on)}$$

• To regulate: $V_{IN} \geq V_{OUT} + V_{dropout}$

• If $V_{IN} < V_{OUT} + V_{dropout}$, the error amplifier saturates $\rightarrow$ no regulation

$$V_{OUT} = V_{IN} - I_o R_{DS(on)}$$


• Efficiency: $P_{loss} = (V_{IN} - V_{OUT}) I_o \rightarrow \eta = \frac{V_o}{V_{IN}}$

• high current / high $V_{IN} - V_{OUT} \rightarrow$ high power loss


III. Switching Regulators

• energy flow is controlled through the ON/OFF states of transistors and transferred through inductors and capacitors


Buck Converter (Step-Down)

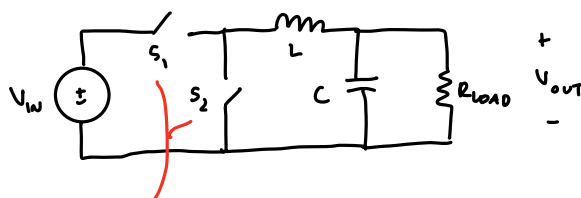

PWM Control

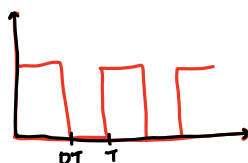


Boost Converter (Step-Up)

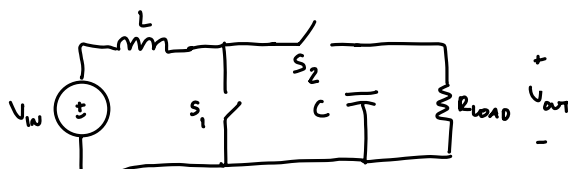

Buck Converter Analysis:


State 1: S_1 ON + S_2 OFF

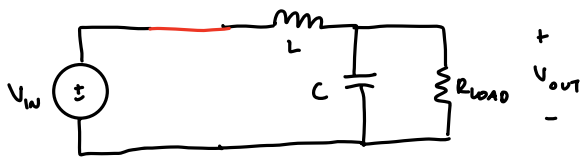

$$V_{L_1} = V_{IN} - V_{OUT}$$

• i_L increases

State 2: S_2 ON + S_1 OFF

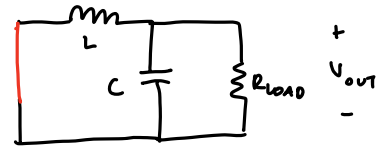

$$V_{L_2} = -V_{OUT}$$

• i_L decreases

In steady-state, $\langle V_L \rangle = 0$.

$$D V_{L_1} + (1-D) V_{L_2} = 0$$


$$D(V_{IN} - V_{OUT}) + (1-D)(-V_{OUT}) = 0$$

$$D V_{IN} - D V_{OUT} - V_{OUT} + D V_{OUT} = 0$$

$$\boxed{V_{OUT} = D V_{IN}} \quad V_{OUT} < V_{IN}$$

Boost Converter Analysis:


State 1: S_1 ON + S_2 OFF

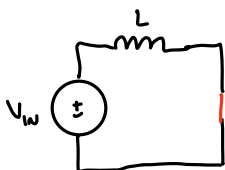

$$V_{L_1} = V_{IN}$$

• i_L increases

State 2: S_2 ON + S_1 OFF

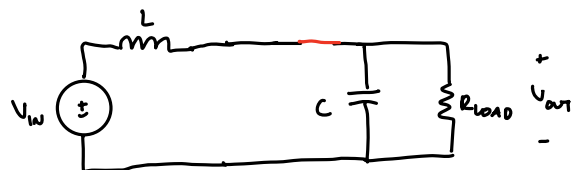

$$V_{L_2} = V_{IN} - V_{OUT}$$

In steady-state, $\langle V_L \rangle = 0$.

$$D V_{L_1} + (1-D) V_{L_2} = 0$$

$$D V_{IN} + (1-D)(V_{IN} - V_{OUT}) = 0$$

$$D V_{IN} + V_{IN} - D V_{IN} - V_{OUT} + D V_{OUT} = 0$$

$$\boxed{V_{OUT} = \frac{V_{IN}}{1-D}} \quad V_{OUT} > V_{IN}$$

• Efficiency: $\sim 90-100\%$


- conduction and switching losses
- internal resistances of L and C

IV. Switching Regulator Waveforms (Buck)

Inductor $v_L = L \frac{di_L}{dt}$

• State 1: $\frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$

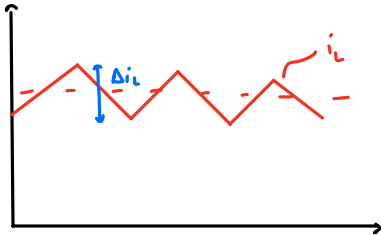
• State 2: $\frac{di_L}{dt} = \frac{-V_{out}}{L}$



$$\Delta i_L = \frac{V_{in} - V_{out}}{L} \cdot D \cdot T_s = \frac{V_{out}}{L} (1-D) \cdot T_s$$

↑
switching period

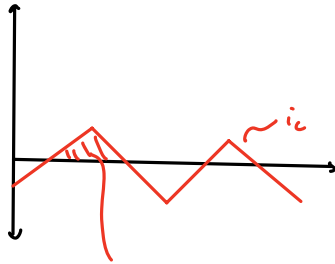Capacitor $i_C = C \frac{dv_C}{dt} = i_L - i_{out}$



$$\Delta Q = \frac{1}{2} \left(\frac{T_s}{2} \right) \left(\frac{\Delta i_C}{2} \right) = \frac{\Delta i_C T_s}{8}$$

$$\Delta Q = C \Delta V \rightarrow \Delta V_C = \frac{\Delta i_C T_s}{8C} \quad \left. \vphantom{\Delta V_C} \right\} \text{output voltage ripple}$$

• Can size inductor and capacitors based on ripple constraints