
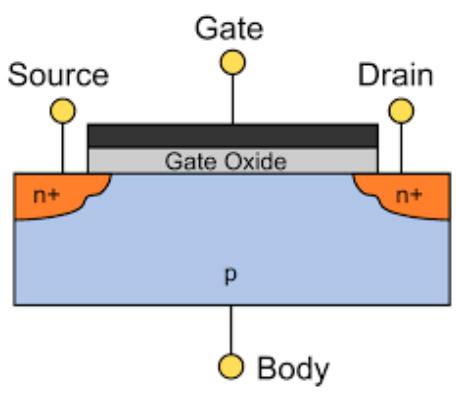


How do fets work?

FET:

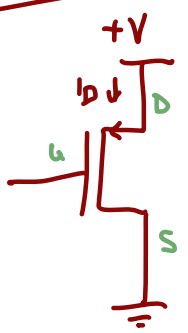

NMOS



$$V_{th} = 0.6V$$


↓  
 $V_{GS}$

$V_{GS} > V_{th}$  : Strong Inversion (essentially on)

$V_{GS} < V_{th}$  : weak inversion

In strong Inversion:

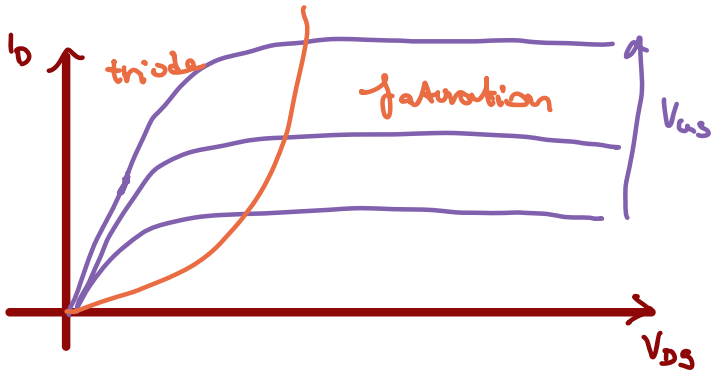Triode Region:  $V_{DS} < V_{GS} - V_{th}$   
 Saturation Region:  $V_{DS} > V_{GS} - V_{th}$



Once it's saturated, changes you make to the voltages you're applying (like  $V_{DS}$ ) won't change  $I_D$  anymore.

$$I_D = \frac{1}{2} \underbrace{\mu_n C_{ox} \frac{W}{L}}_{\text{attributes of the FET}} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

↳ usually 0

But why all of this?


FETs are switches but we can't just flip them like mechanical switches

We tell FETs to be on or off using the gate voltage, making  $V_{GS} > V_{th}$

$$\mu_n C_{ox} \frac{W}{L} = 32 \mu A/V^2 \quad V_{th} = 0.5V$$

$$\lambda = 0$$

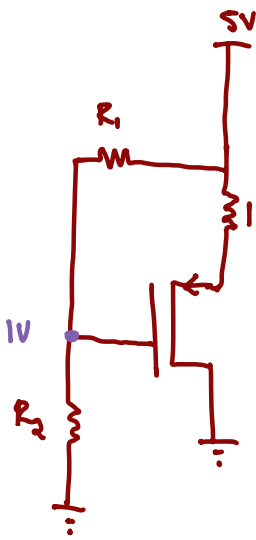Find  $R_1$  and  $R_2$  such that  $I_D = 4 \mu A$



$$V_{GS} = 1V$$

$$V_{th} = 0.5V$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$$= 16 \mu (V_{GS} - V_{th})^2$$

$$4 \mu A = 16 \frac{\mu A}{V^2} (V_{GS} - 0.5)^2$$

$$0.25 V^2 = V_{GS}^2 - V_{GS} + 0.25 V^2$$

$$V_{GS} = 1V$$

Voltage divider:

$$1V = 5V \frac{R_1 R_2}{R_1 + R_2}$$

$$R_1 + R_2 = 5 \frac{R_1 R_2}{R_1 + R_2}$$

$$R_1 = 1k\Omega$$

$$1k\Omega + R_2 = 5k(R_2)$$

$$R_2(5k - 1) = 1k\Omega$$

$$R_2 = \frac{1k\Omega}{4.999k} = 0.2\Omega$$