

# Lecture 04 - TOPOLOGIES


## Common electrical topologies (2/2)

# Outline

- Introduction
- LDO Regulators
- Buck and Boost Converters
- ESP Module
- Switches and Potentiometers
- Display and Shift Registers
- Summary


# Introduction

## Block Diagram

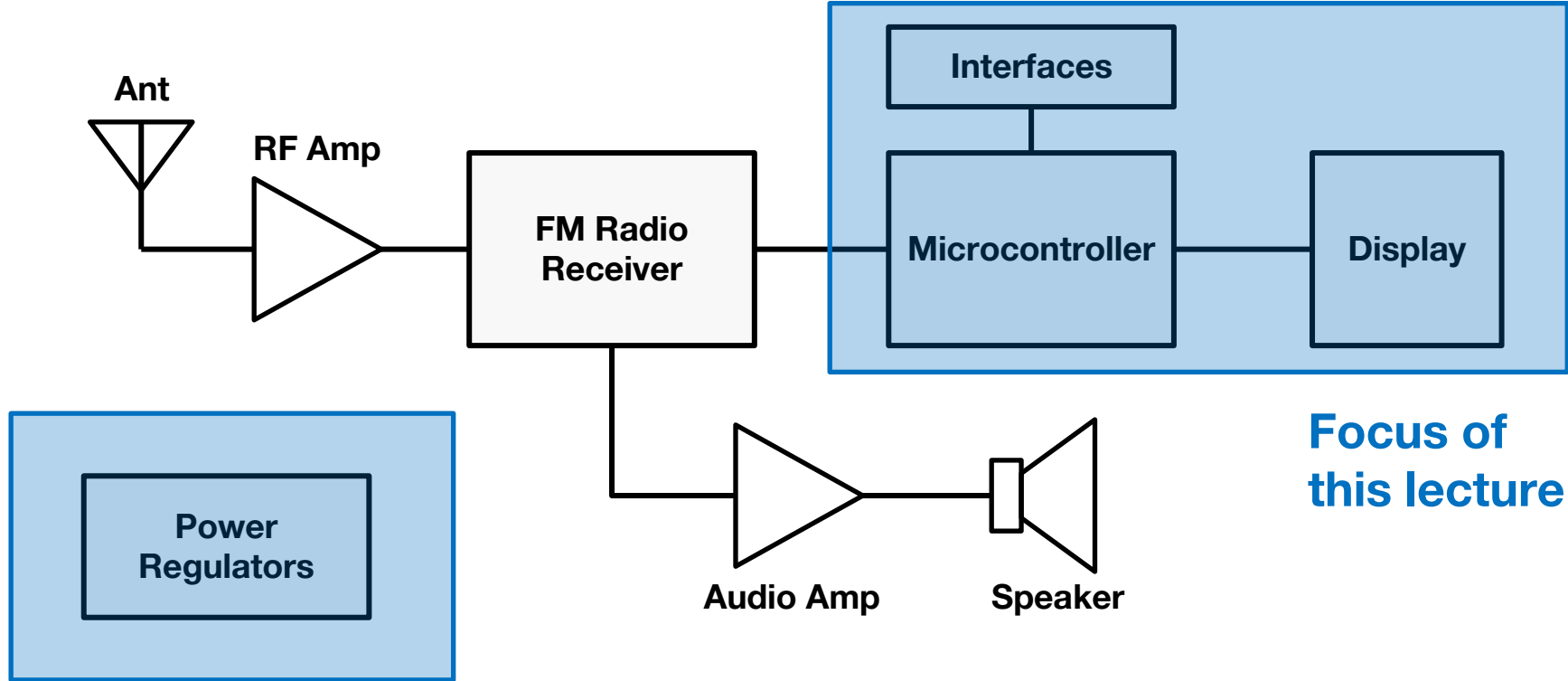

# Low Dropout Regulators (LDOs)

## Power Regulation

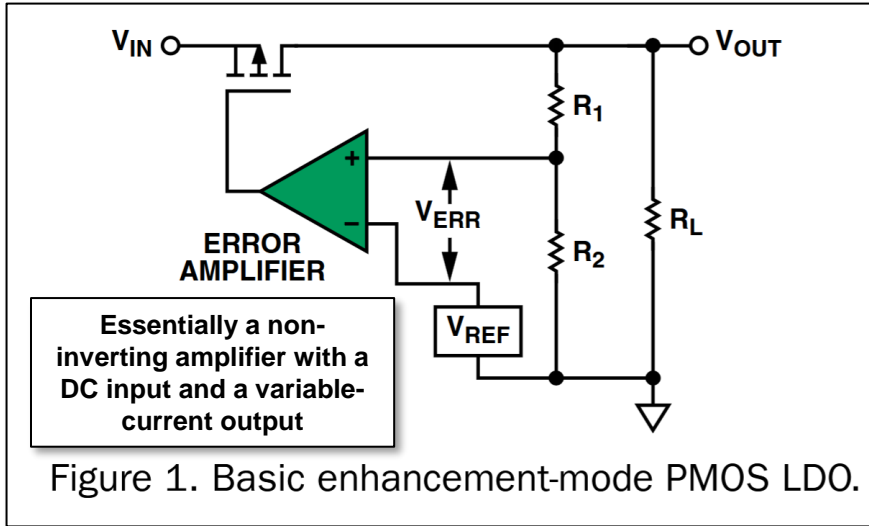

$R_1$  and  $R_2$  form a voltage divider feedback network that amplifies  $V_{REF}$  to provide a variable voltage output

LDOs are crucial for their low noise and simplicity

- No switching occurs
- Small size (no large inductors required)
- Cheaper

LDOs, however, cannot be used for all applications:


- Cannot boost voltages
- Lossy (requires heatsinking)
- In order to bias output transistor, a dropout voltage is required (0.1 V to 2 V depending on topology)

Typically, LDOs should be preferred for use in for low-noise and/or low current voltage step-down applications

# Switching Converters

## Schematics


### Buck Converter

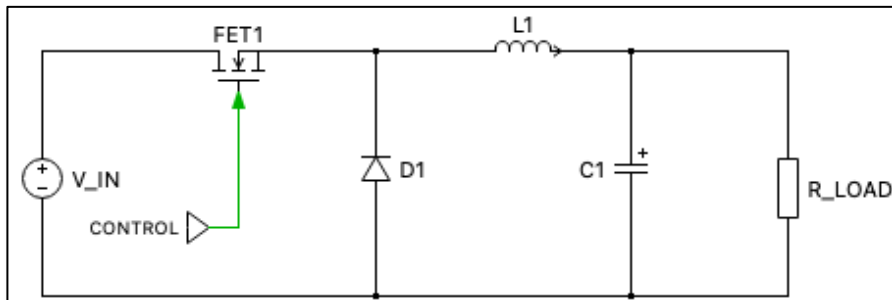

#### Step-Down Converter

output voltage = duty cycle  $\times$  input voltage

### Boost Converter

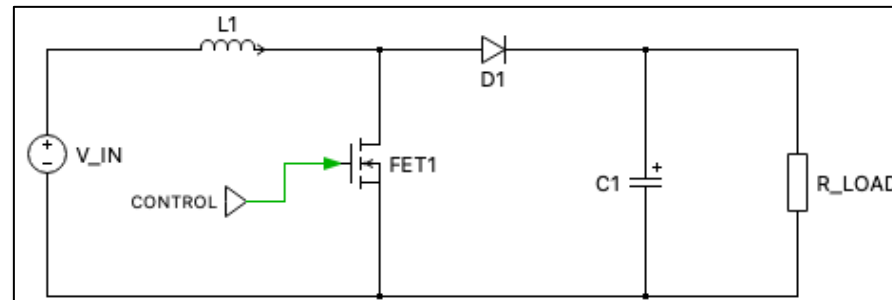

#### Step-Up Converter



output voltage = input voltage  $\div$  (1 - duty cycle)

# Switching Converters
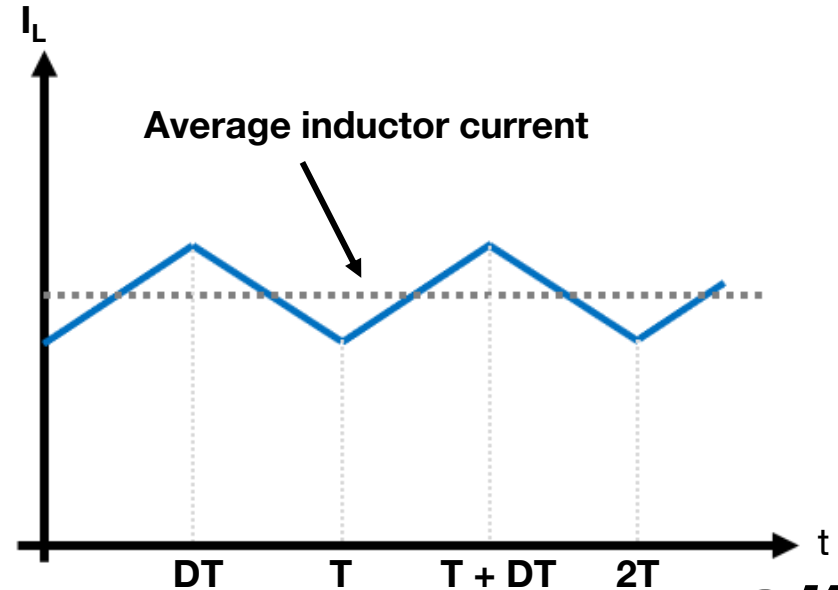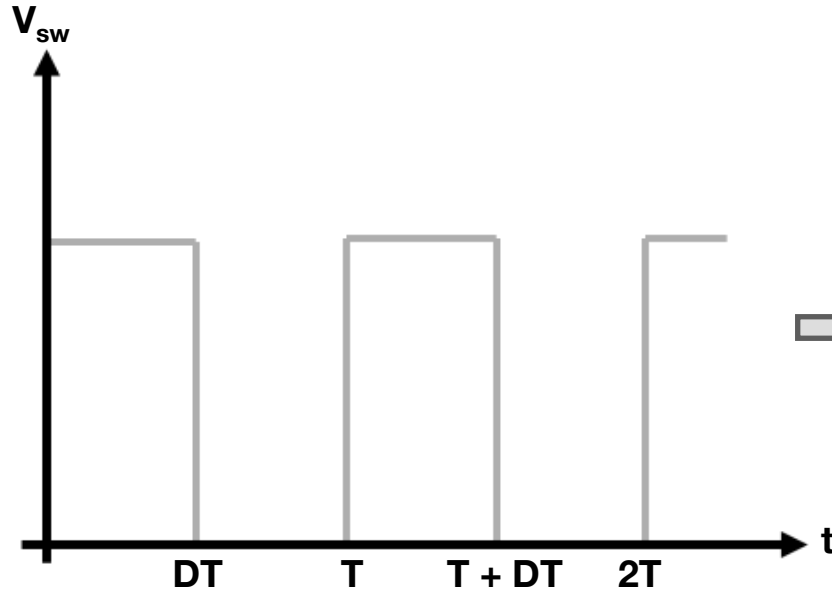
## Control

The FET of the converter is controlled via PWM, where the duty cycle determines the ratio between the input voltage and the output voltage


This causes the current across the inductor to ramp up and ramp down, which in conjunction with the capacitor, provides a voltage to the load



# Switching Converters


## Buck Converter Operation

### MODE 1: Switch On

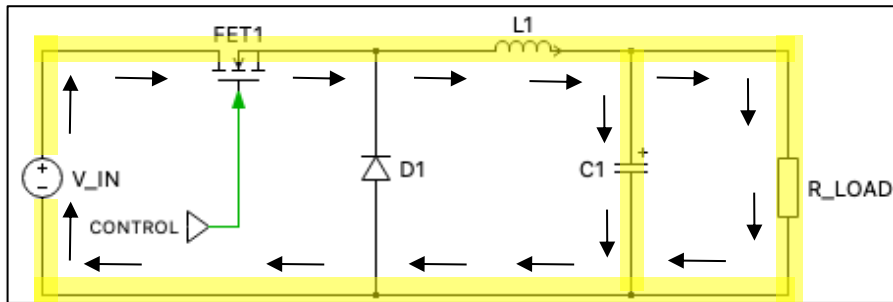

When the switch is turned on, positive voltage is forced across the inductor, causing the current to increase. This inductor current flows through the capacitor and the load.

### MODE 2: Switch Off

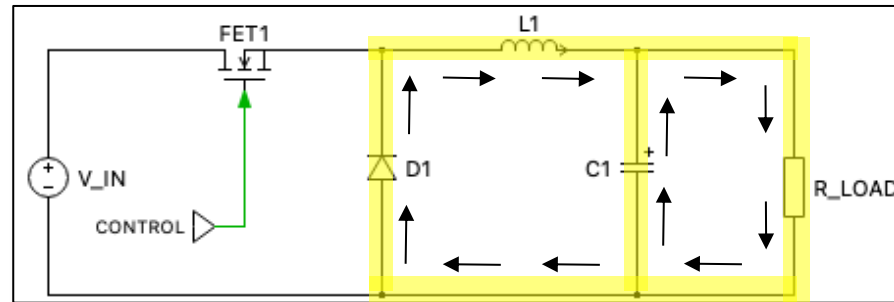


When the switch is turned off, the inductor current decreases, forcing a negative voltage across the inductor and turning on the diode. The capacitor discharges into the load as well.

In a buck converter, the load current is the average inductor current.

# Switching Converters


## Boost Converter Operation

### MODE 1: Switch On

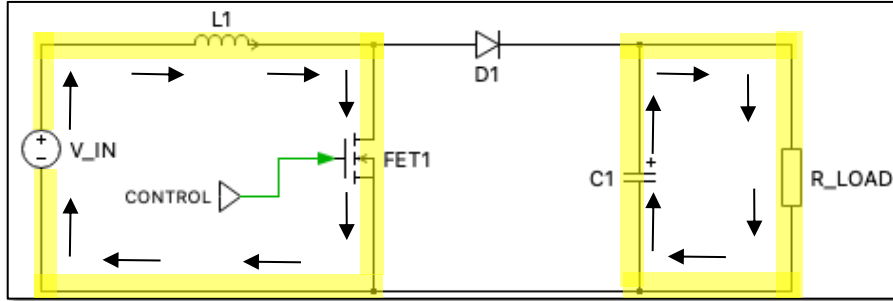

When the switch is turned on, positive voltage is forced across the inductor, causing the current to increase. The capacitor supplies current to the load in isolation.

### MODE 2: Switch Off

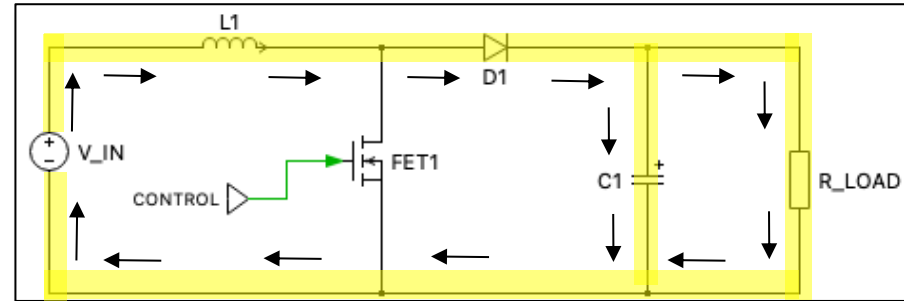

When the switch is turned off, the inductor current decreases, forcing a negative voltage drop across the inductor. This causes the capacitor voltage, and in turn the load voltage, to increase beyond the input voltage.

In a boost converter, the load current is the average diode current.



# ESP32 Module

## The Brains of Our Circuit

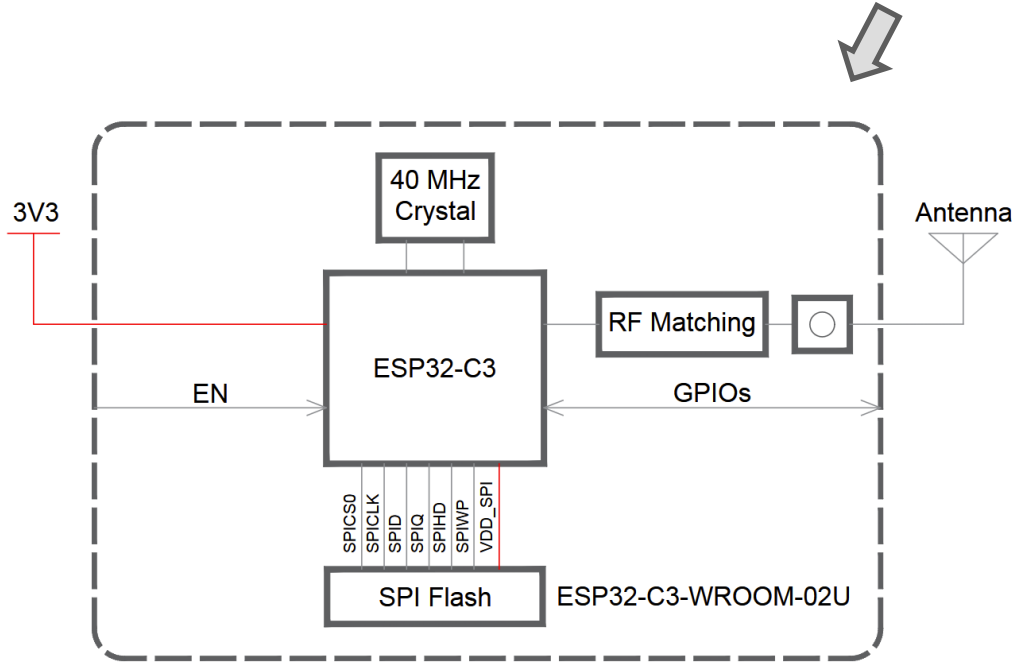



Figure 2: ESP32-C3-WROOM-02U Block Diagram

The ESP32-C3-WROOM-02U module conveniently houses the peripheral circuits needed to support the ESP32-C3 microcontroller, such as:

- **Crystal oscillator** – required to set the clock frequency and timing of the microprocessor
- **SPI flash** – to provide extra off-microcontroller storage for collected data or programs
- **GPIO fanouts** – makes routing to the GPIO pins much easier
- **RF matching** – for the WiFi/Bluetooth functionality
- **Metal housing** – for environmental and EMI shielding

# ESP32 Module

## Functionality

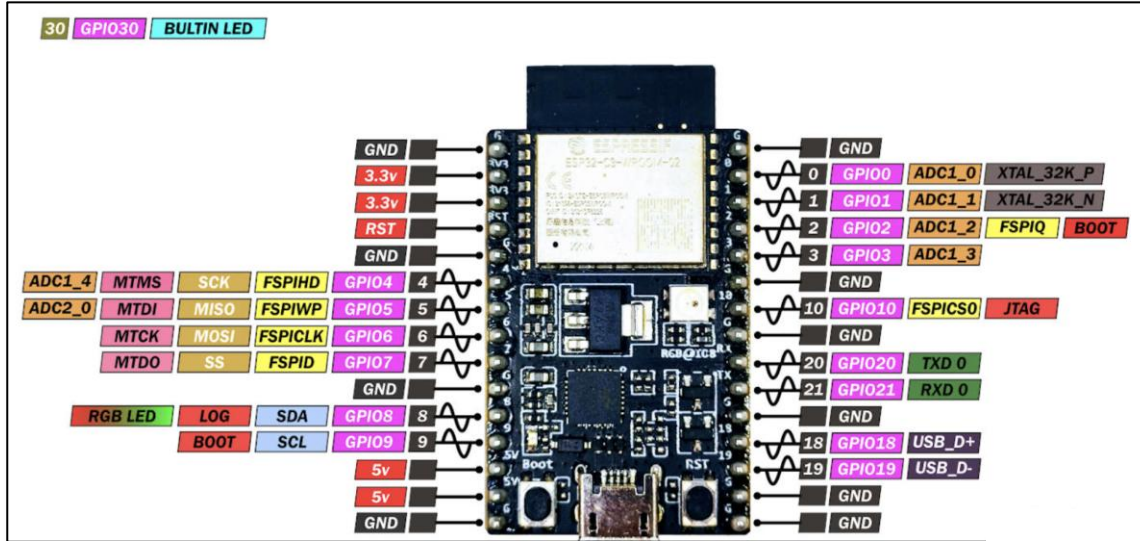

32 pins, several with multiple potential functions including:

- Power (3.3V and 5V power rails)
- GPIO
- USB data lines
- SPI functionality
- UART functionality
- I2C and I2S functionality
- ADC channels
- LED PWM Control


# Switches

## Types of Switches

### SPST

Single-Pole, Single-Throw

...aka one input, one output

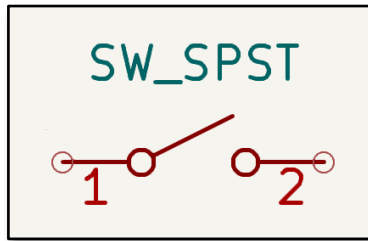


Schematic  
Symbol



### SPDT

Single-Pole, Double-Throw

...aka one input, two outputs

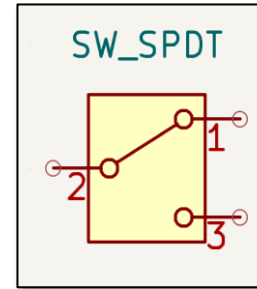


Schematic  
Symbol




# Potentiometers

## Variable Resistors


### Symbol

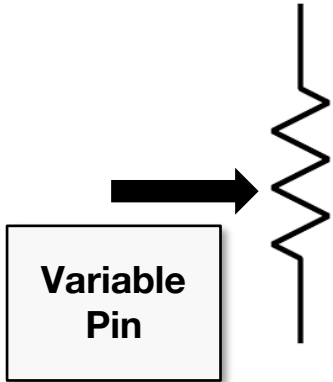

### Pinout

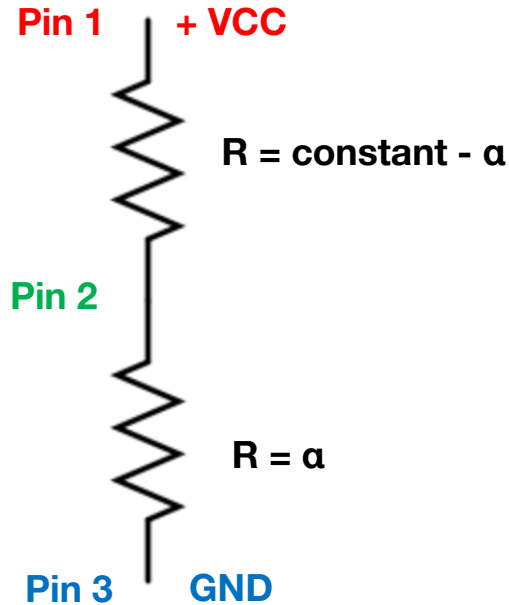




### Example Circuit

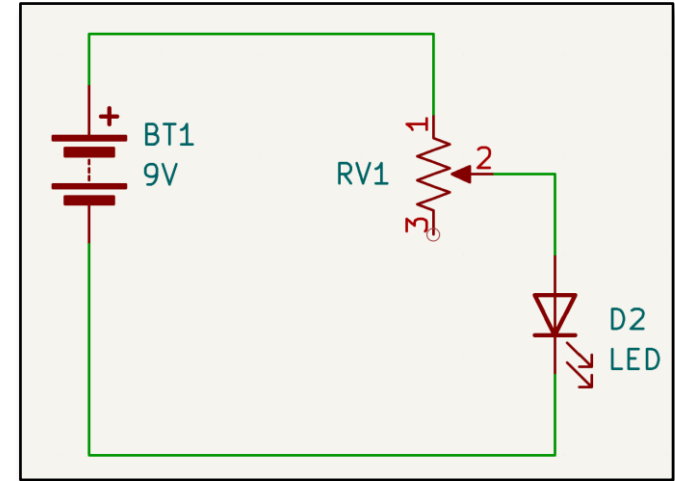

Adjustable-brightness LED!

# Display

## 7-Segment Display

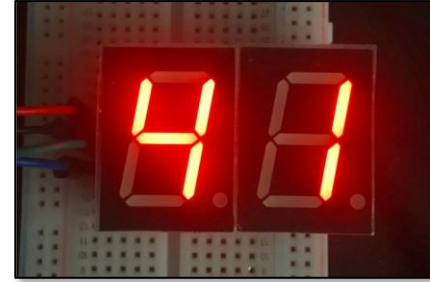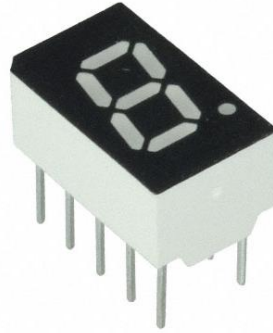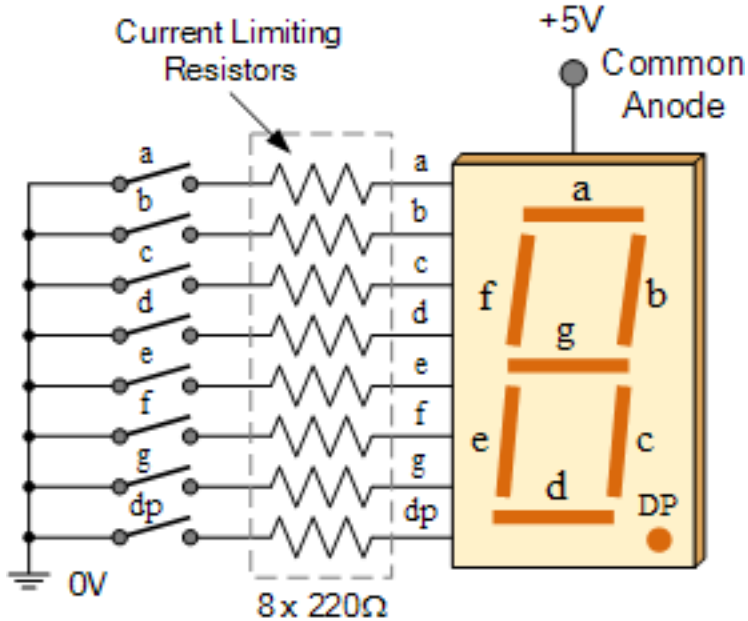

7-Segment displays are commonly used for displaying numbers (and some letters).

- Consists of 7 individually addressable LEDs


If we decide to use four 7-segment displays for our FM radio to display tuned frequency (e.g., 101.5), that requires digital control of  $4 \times 7 = 28$  pins!

But our ESP32 microcontroller only has 13 general-purpose input/output (GPIO) pins...  
How do we control of the LEDs?

# Shift Registers
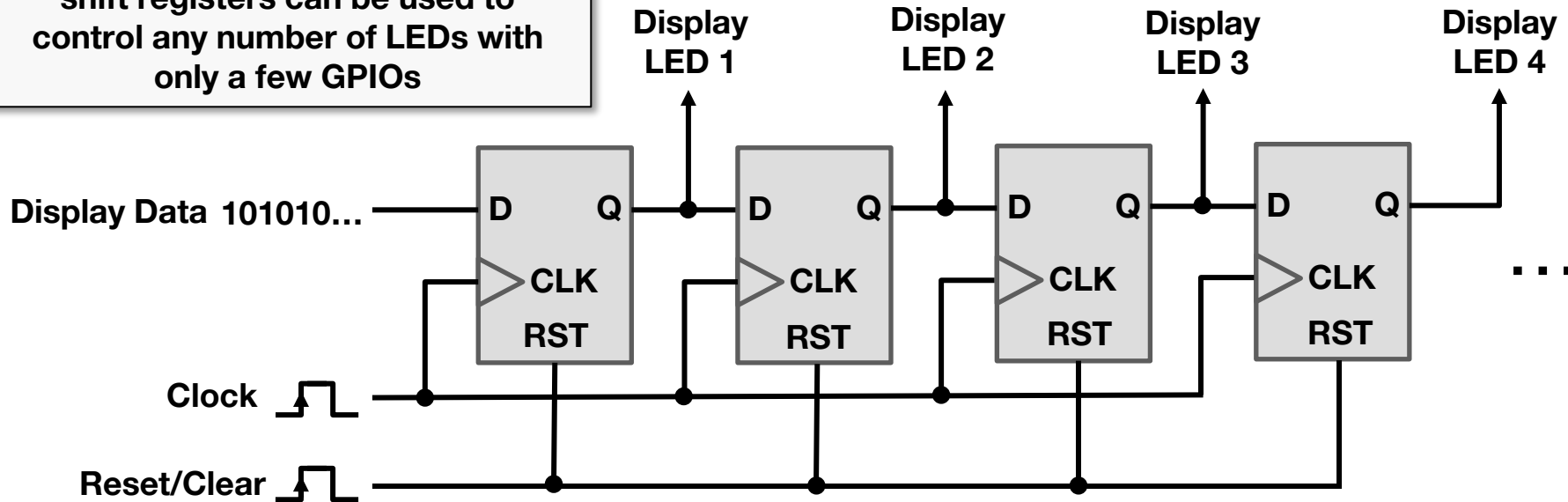
## Digital Control


A chain of Serial-In, Parallel-Out shift registers can be used to control any number of LEDs with only a few GPIOs



Good solution for increasing number of digital outputs, given outputs that do not change often

# Summary

## Block Diagram, Revisited

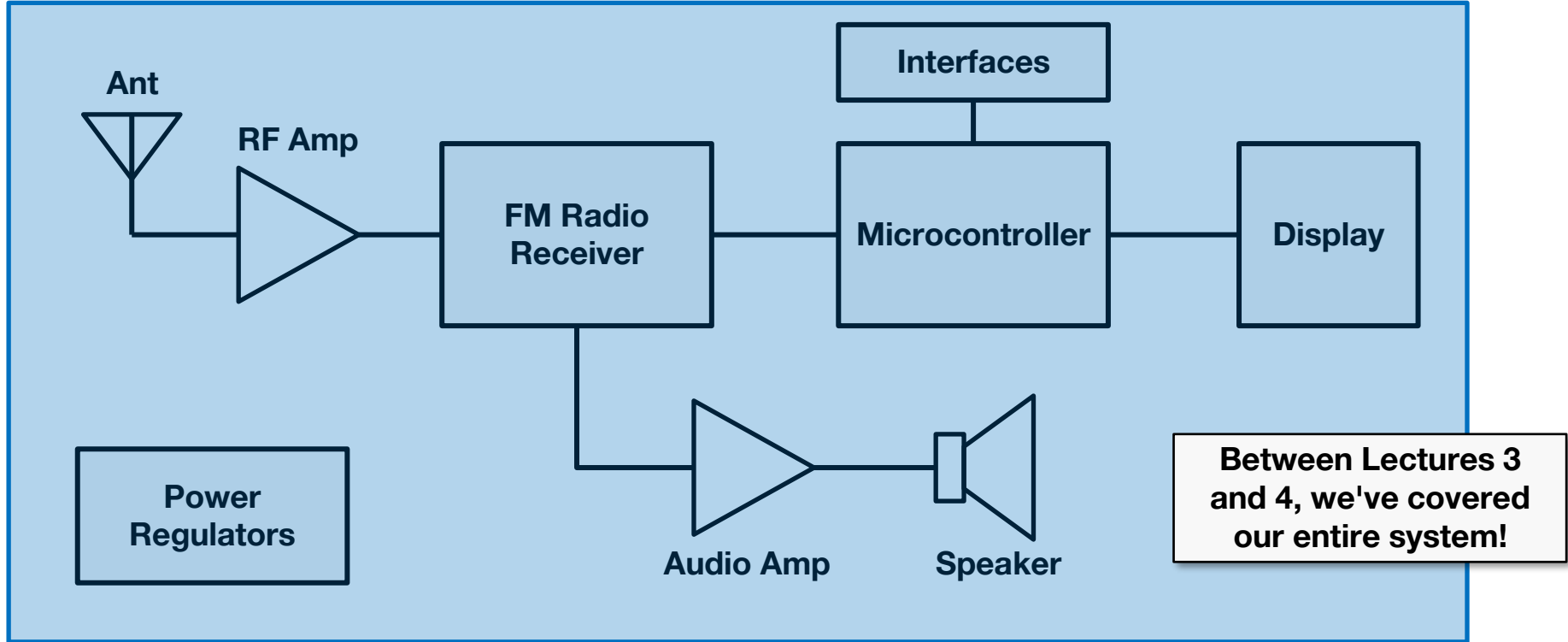

# Questions?