

lecture 5 - DEBUGGING!

Electrons, often don't like doing what they're told. **Now we want to use our advanced electrical engineering knowledge to figure out how and why they may be unhappy!**


- 1) **subject evals!**
- 2) **DR Signups!**

Interrogating your Circuit



◀!— w/ Agent Rick Dicker ofc —>

STEP 1 – let's understand the system

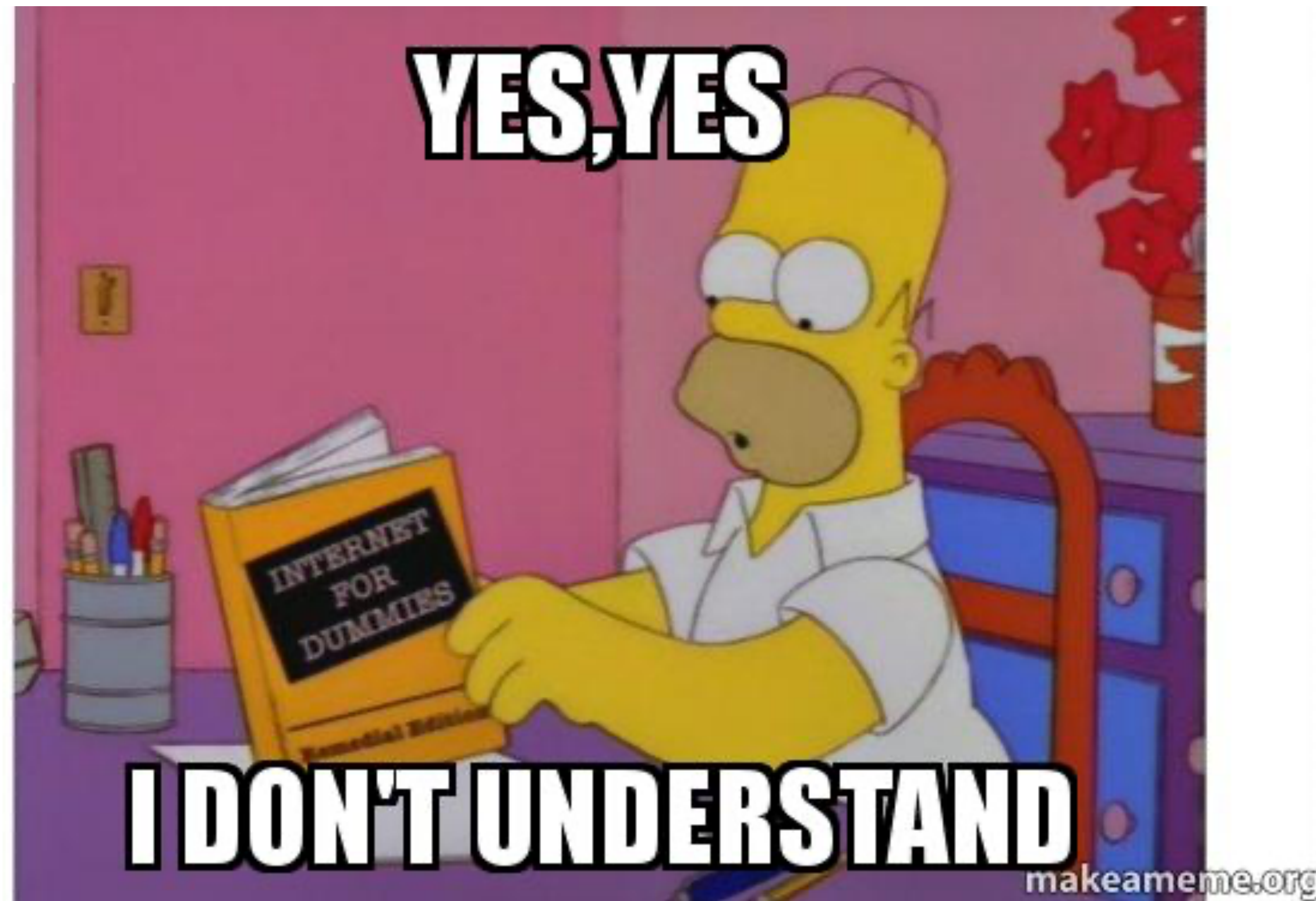

What does a BMS Do?

What does a BMS Do?

E1 - E-Stop

E2 - Under-voltage Lockout


E3 - Overvoltage Lockout

E4 - Overcurrent Lockout


E5 - Overtemperature Protection

E6 - Communications Error


What does a BMS Do?

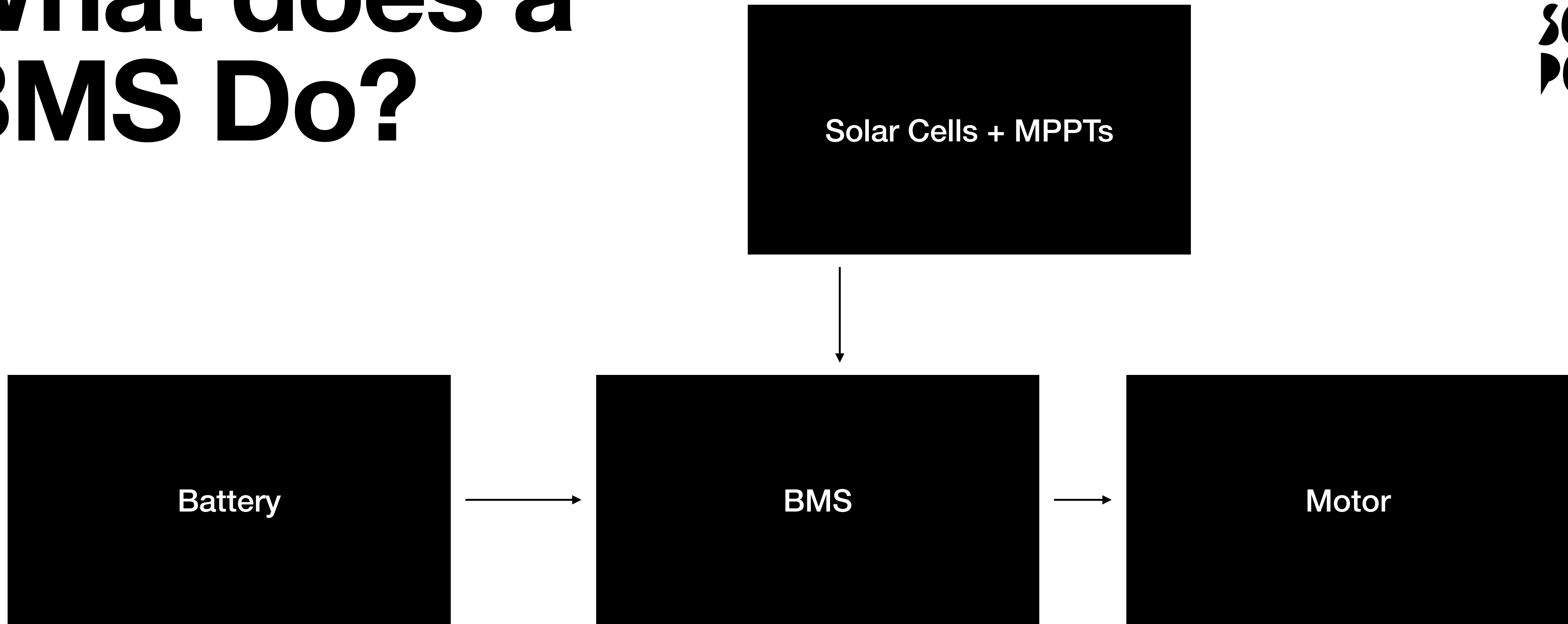

What does a BMS Do?

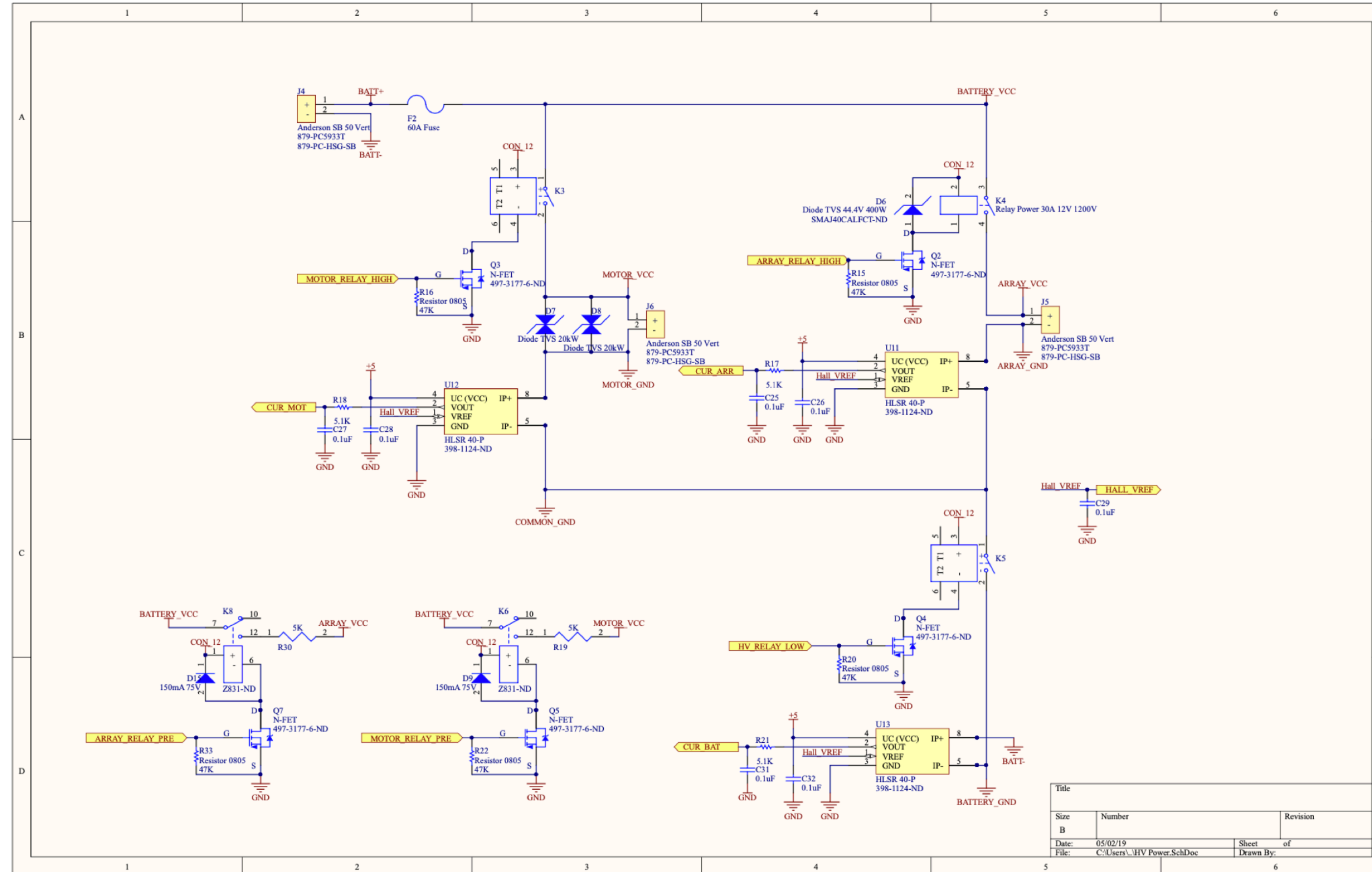

STEP 2— identify the problem

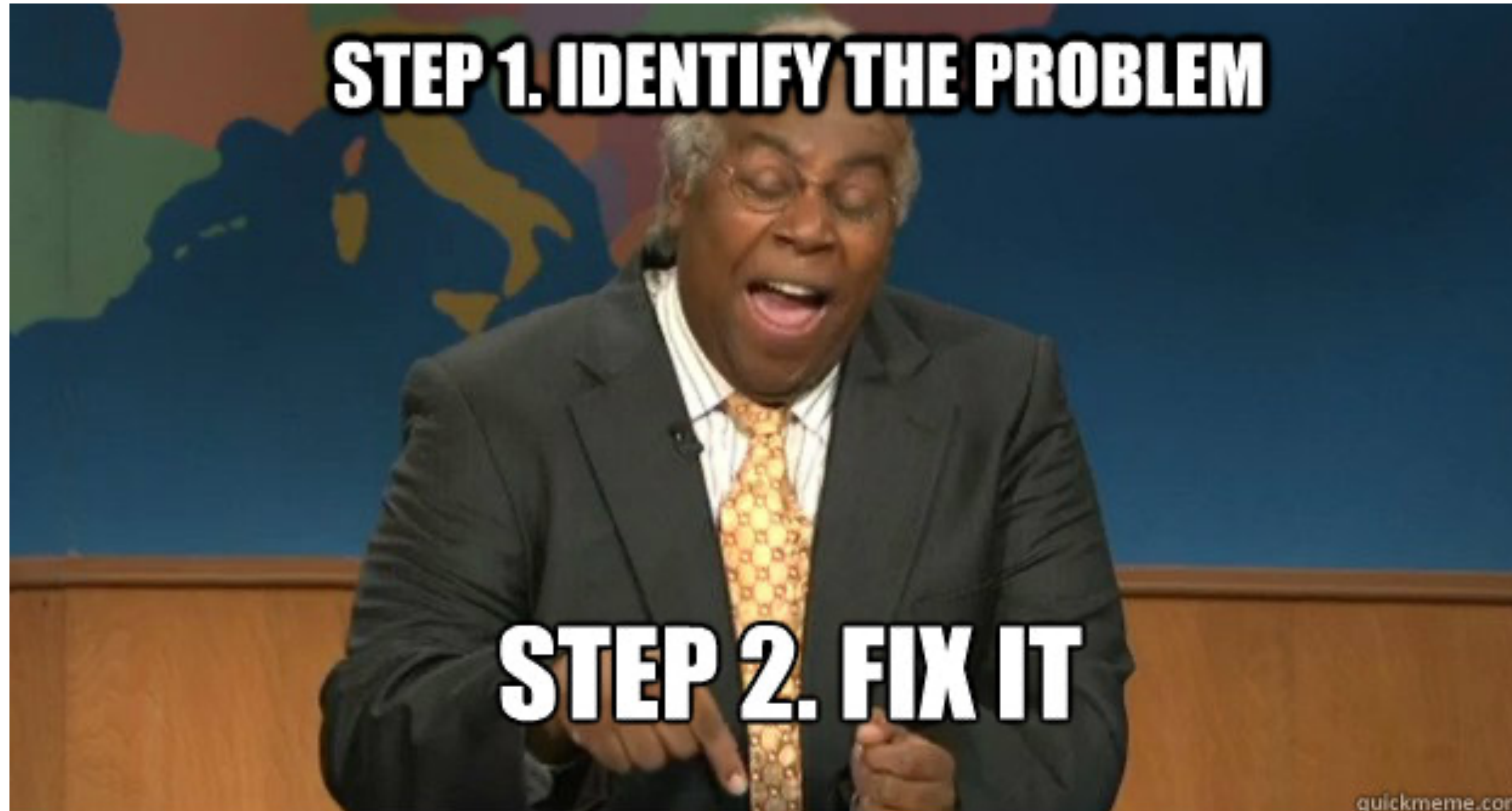

Ok so what if I told you...

Ok so what if I told you...

1) I plugged in the battery to the car...

Ok so what if I told you...


- 1) I plugged in the battery to the car...
- 2) I turned on the car...

Ok so what if I told you...

- 1) I plugged in the battery to the car...
- 2) I turned on the car...
- 3) I IMMEDIATELY got an E4 error

WHAT DO I
DOOOOOOOOO??????????

I CRY EVERY TIME

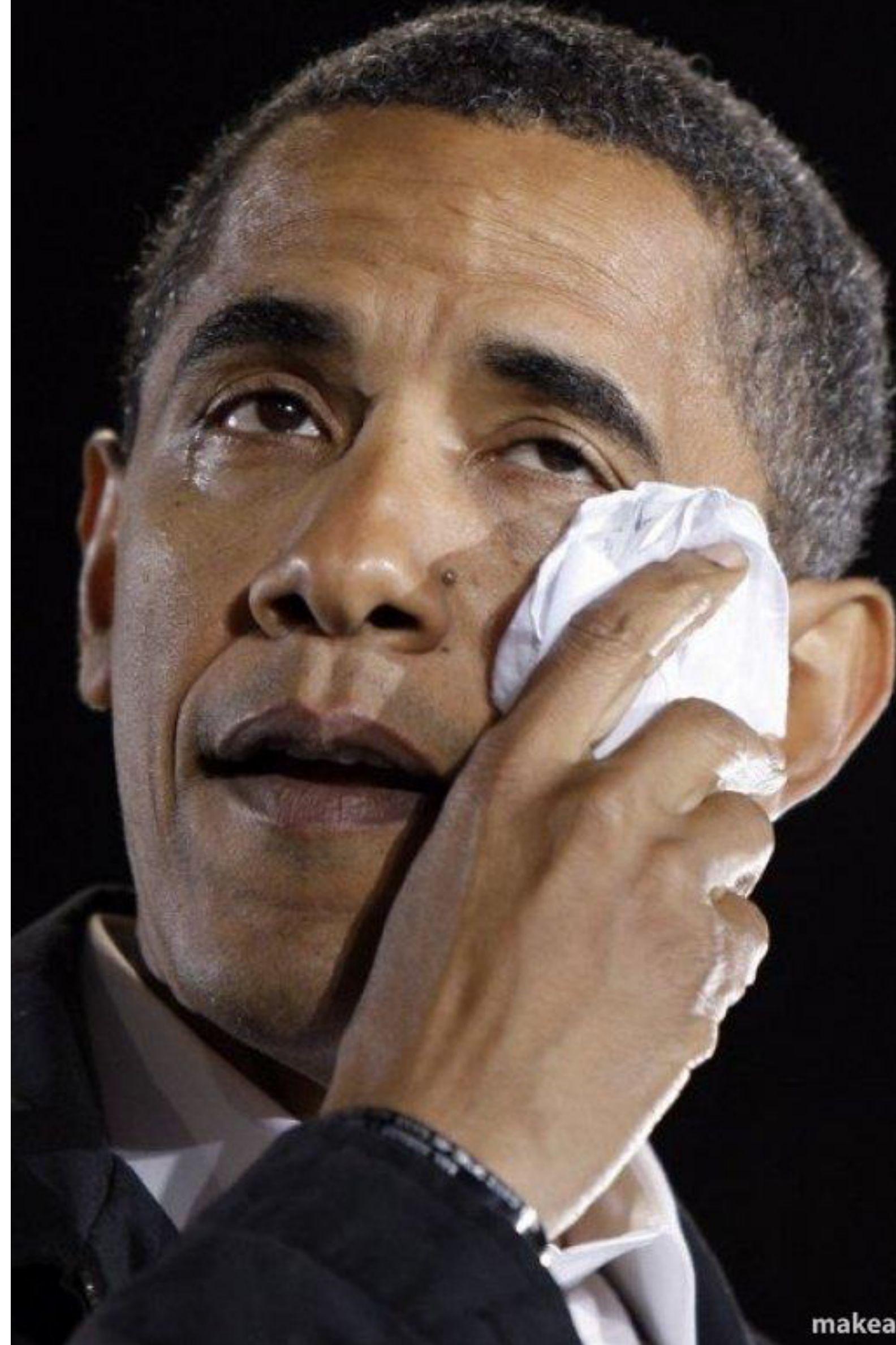

**Ok let's do some debugging on the board
pull up the schematic from here —> [https://
pcb.mit.edu/lectures/lab_02/headboard.pdf](https://pcb.mit.edu/lectures/lab_02/headboard.pdf)**

Step 1 → unplug the array + motor + plug them in one at a time

Step 1 —> unplug the array + motor + plug them in one at a time

Just motor, no E4?

Something going on w/ the Array, MPPTs, or array power circuit

Just Array, no E4?

Something going on w/ the Motor controller, or motor power circuit

Step 1 → unplug the array + motor + plug them in one at a time

Just motor, no E4?

Something going on w/ the Array, MPPTs, or array power circuit

Just Array, no E4?

Something going on w/ the Motor controller, or motor power circuit

We get E4 when the array is plugged in if the motor is ON, or they the array is ON, but not if they're both OFF!

Step 1 —> unplug the array + motor + plug them in one at a time

Array
circuitry is
the issue

Step 2 —> probe output
of MPPTs

Probed output of
MPPTs is NOT OK

Array is the Issue

Just Array, no E4?

Something going on w/
the Motor controller, or
motor power circuit

Probed output of
MPPTs is OK

BMS is the Issue

Step 1 —> unplug the array + motor + plug them in one at a time

Array circuitry is the issue
→

Step 2 —> probe output of MPPTs

Probed output of MPPTs is NOT OK
→


Array is the Issue

↓
Just Array, no E4?

Something going on w/ the Motor controller, or motor power circuit

↓
BMS is the Issue

BMS is the Issue

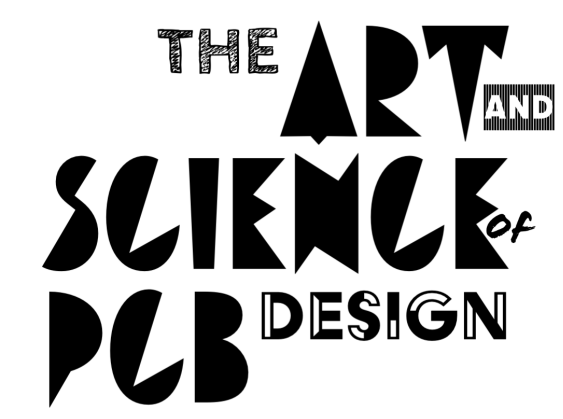

Step 1 → unplug the array + motor + plug them in one at a time

Array circuitry is the issue

Step 2 → probe output of MPPTs

Probed output of MPPTs is NOT OK

Array is the Issue



Just Array, no E4?

Something going on w/ the Motor controller, or motor power circuit



BMS is the Issue

Look @ the Schematic!


BMS is the Issue

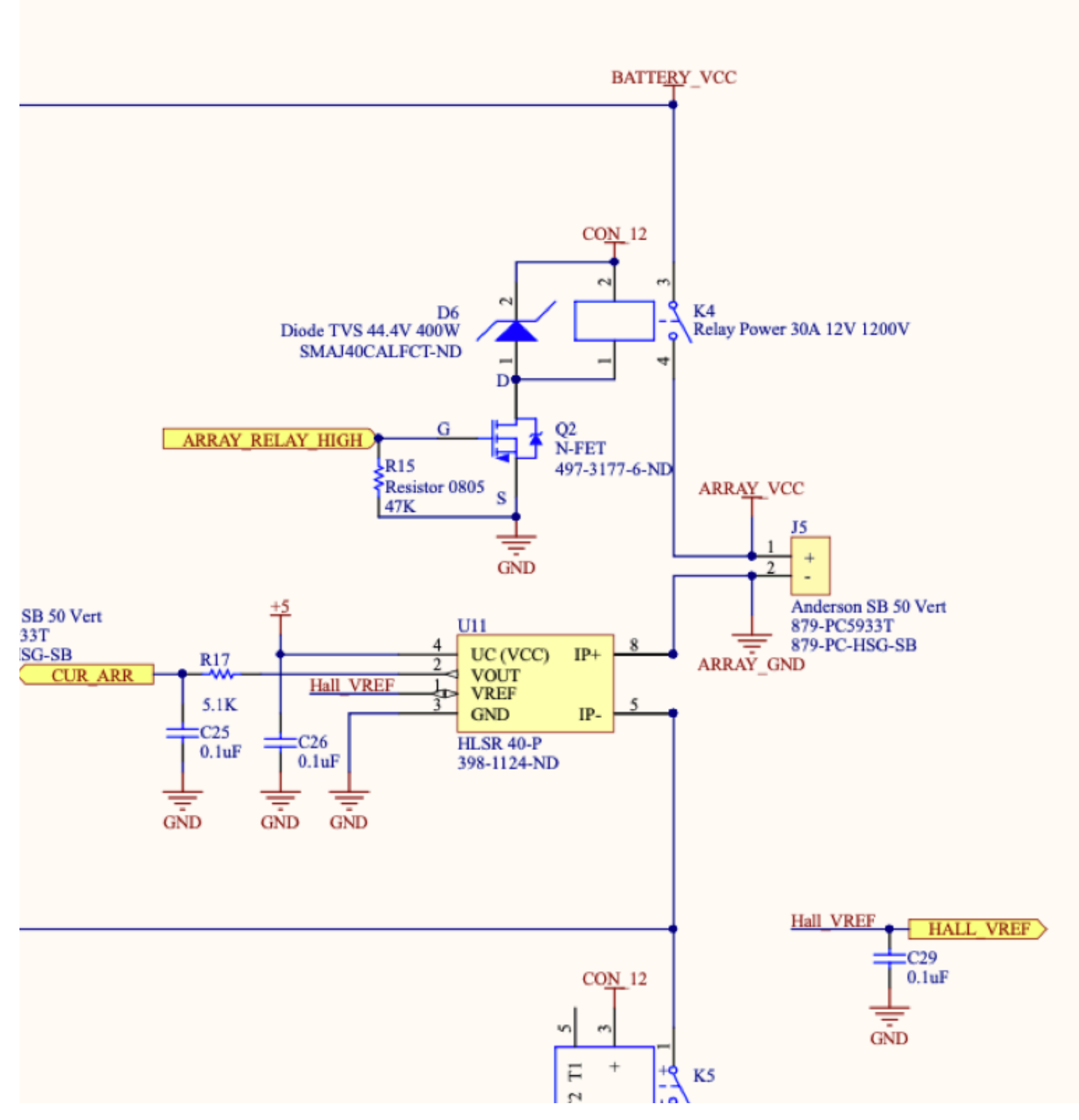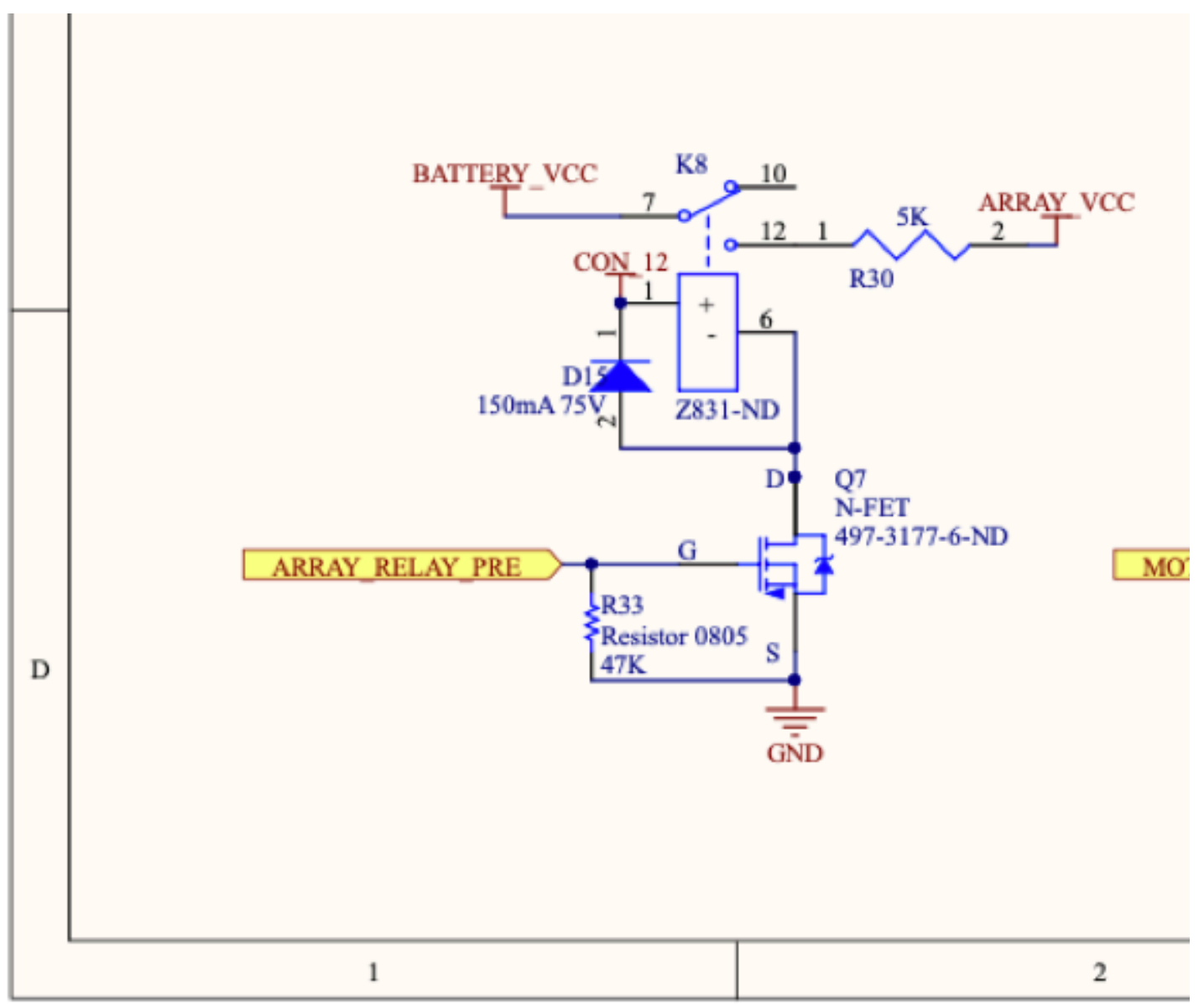



Ok so let's think...

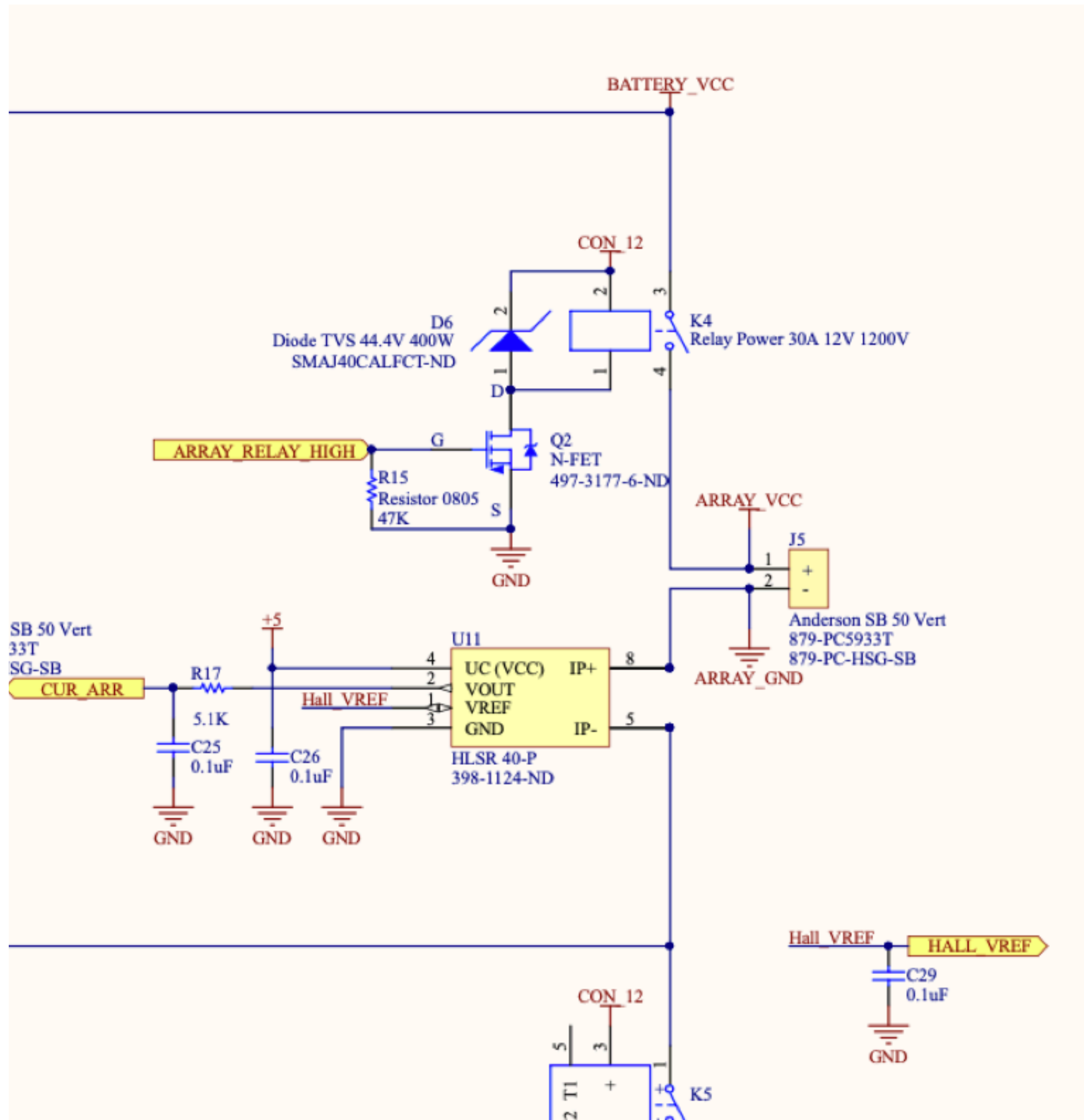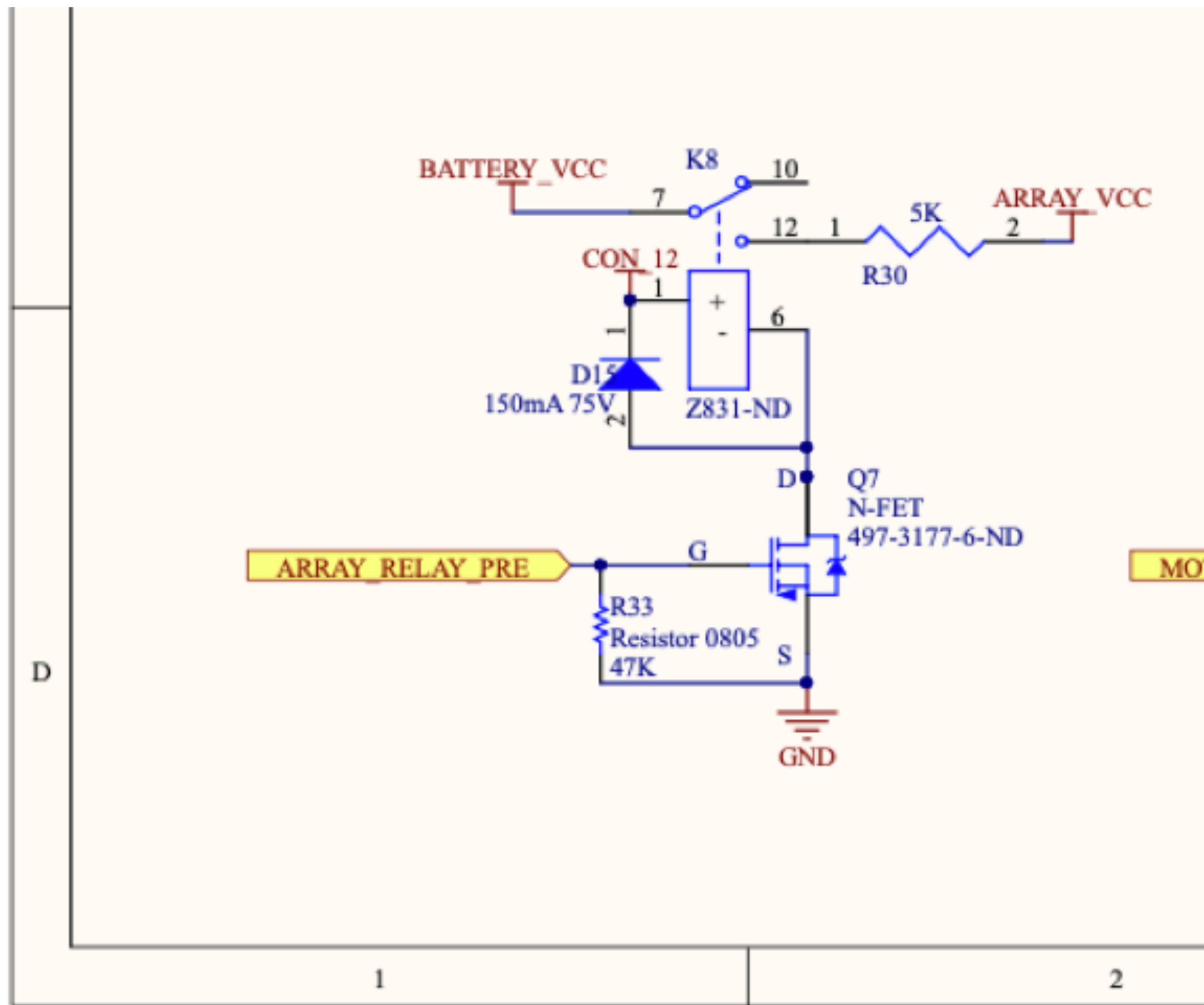


Ok what IS this circuit?

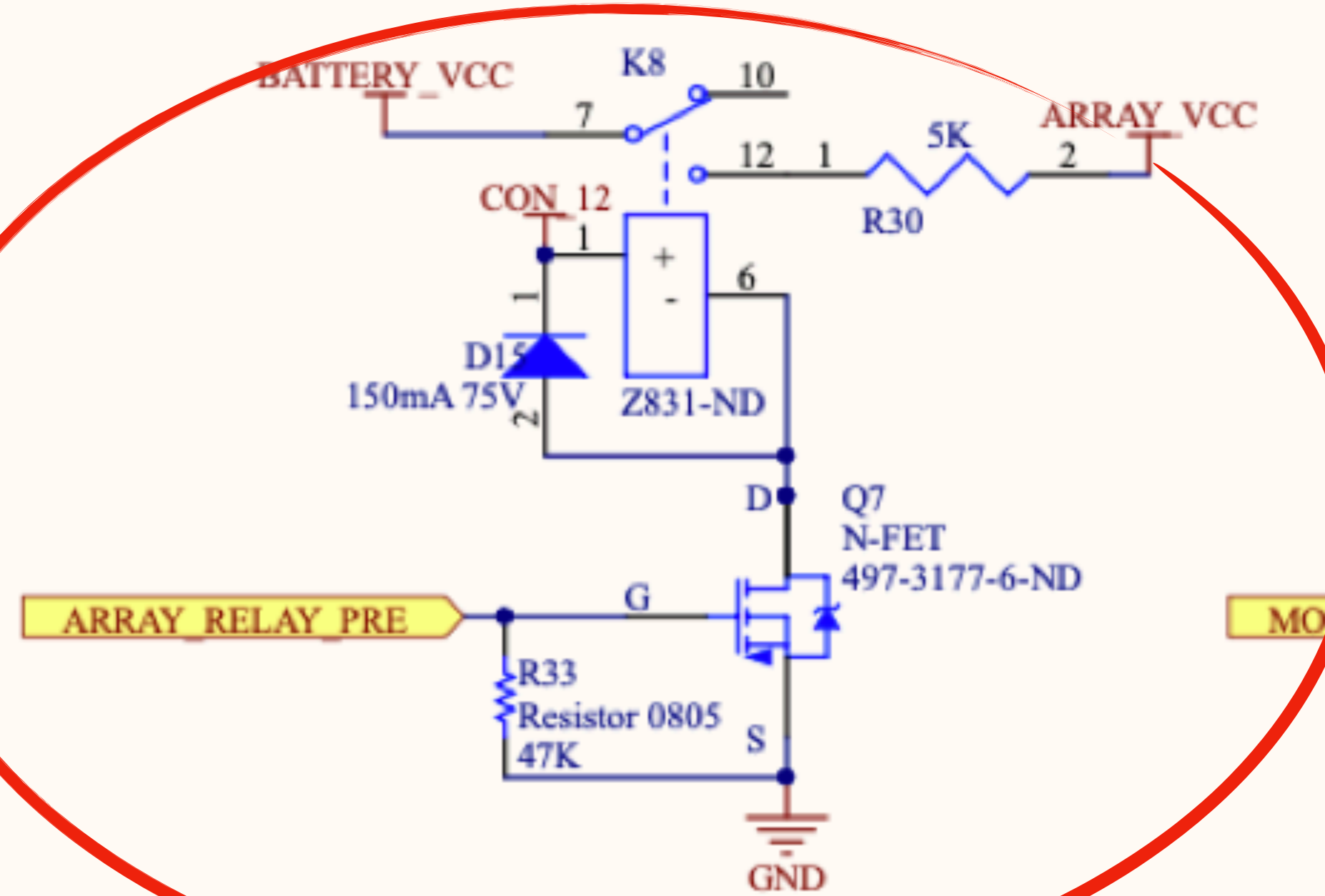


Can something be wrong with this?

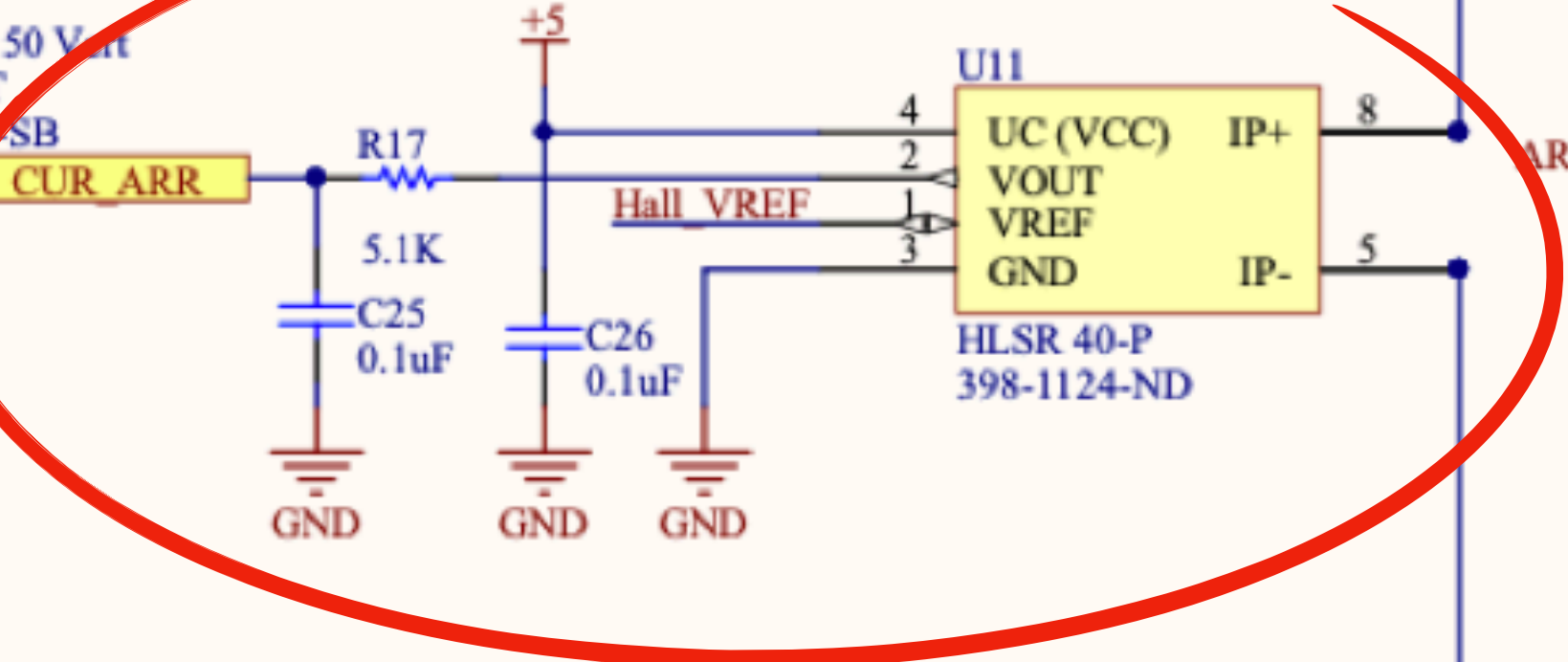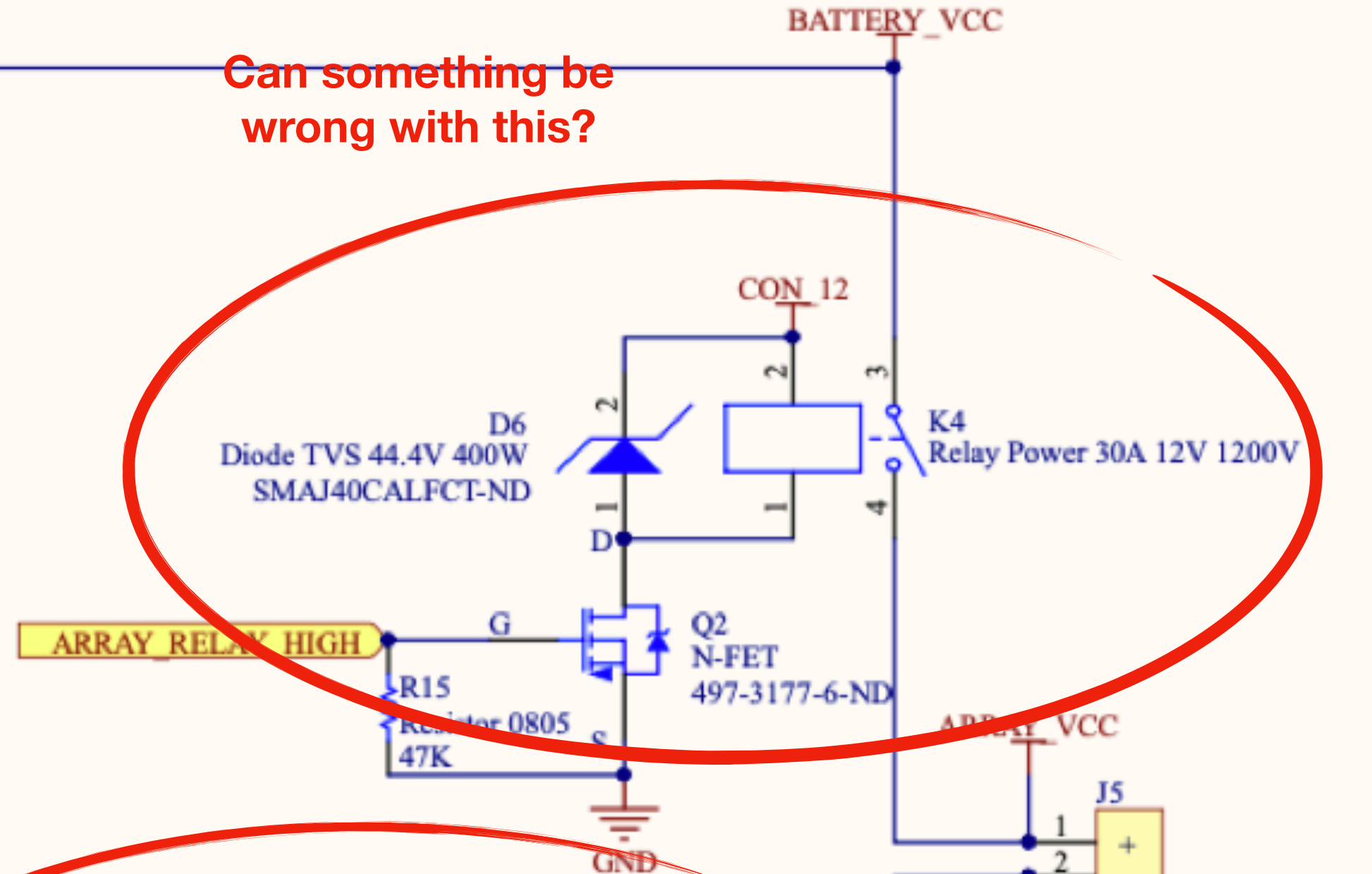

What about this?

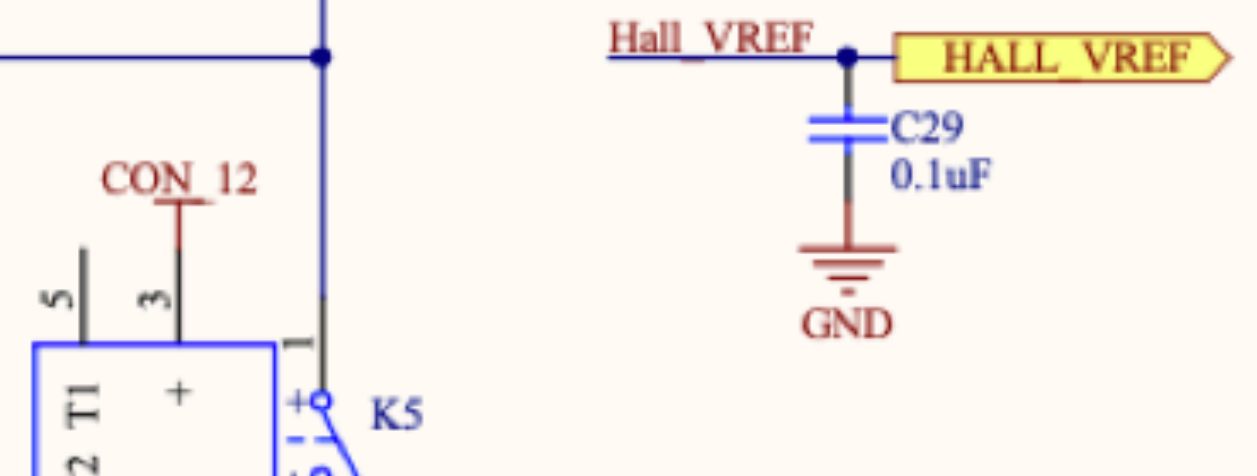


Ok what IS this circuit?

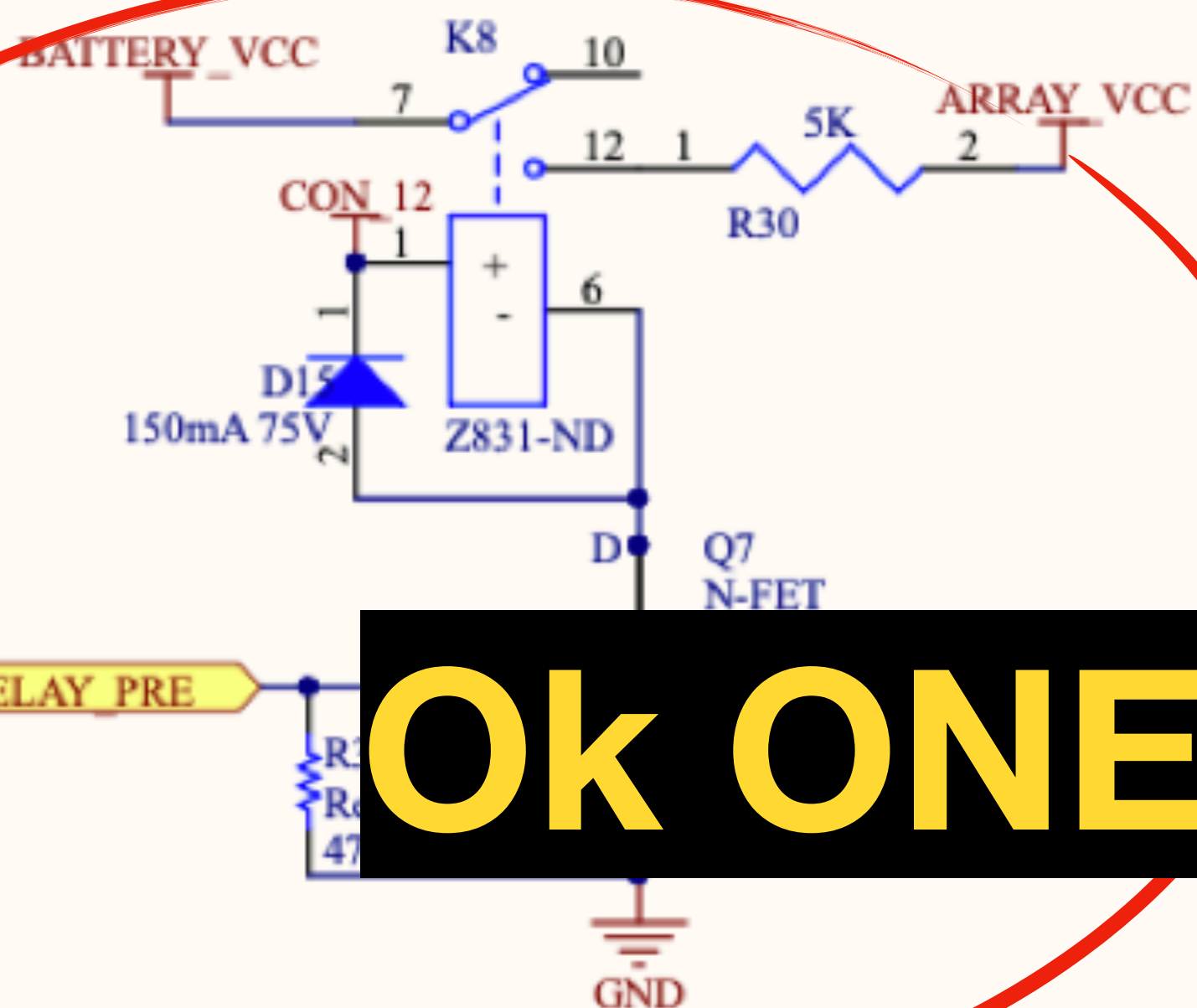


OK ONE AT A TIME!

Can something be wrong with this?

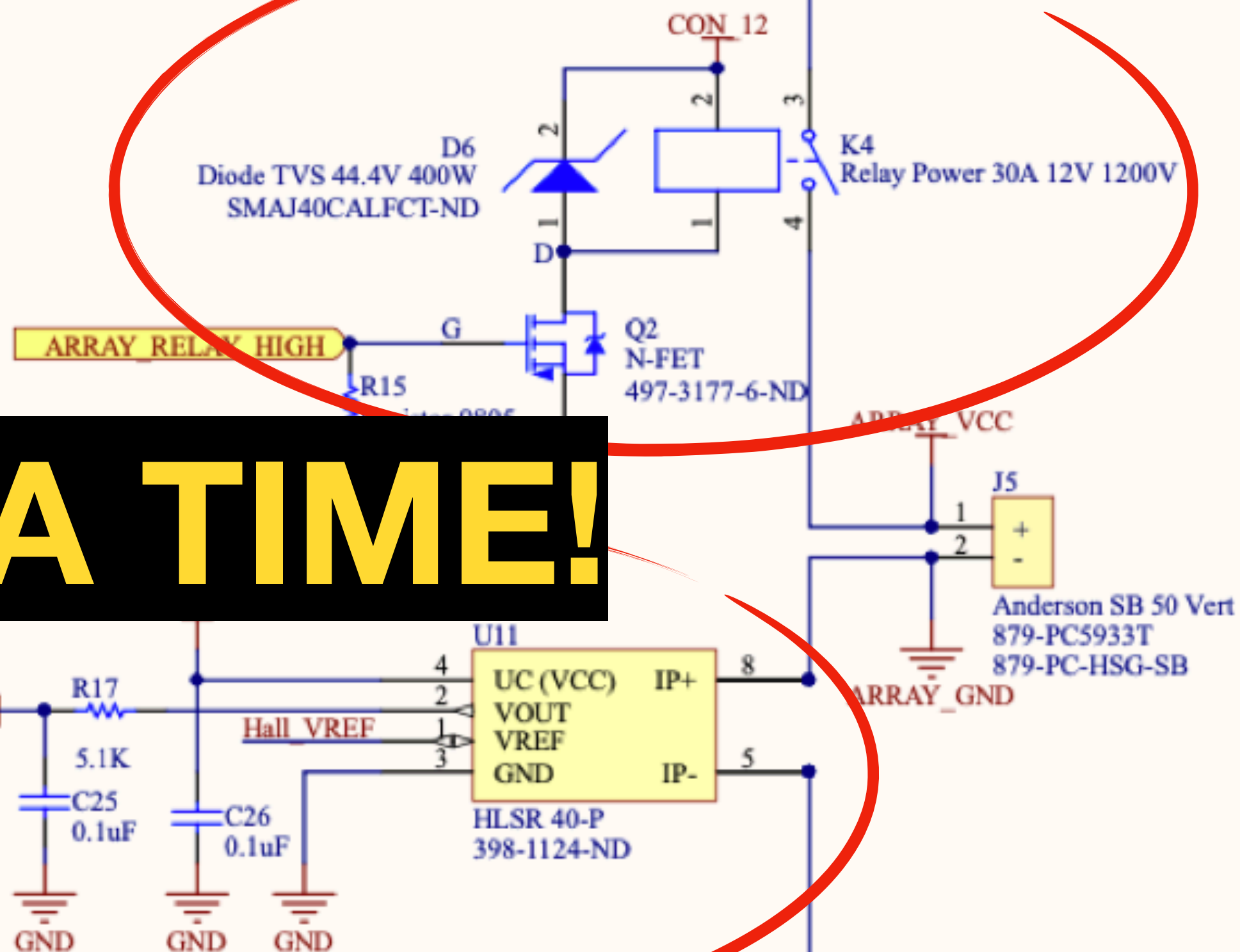


What about this?

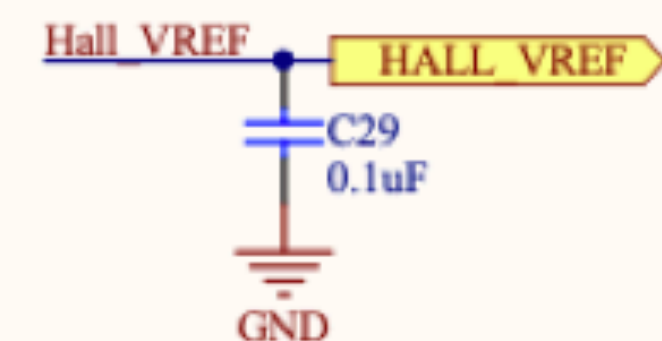

Let's talk about how each of these three circuits work in detail.

- **What's pre-charge?**
- **What's a relay?**
- **What's a contractor?**
- **How does a current sensor work?**

This is a PRE-Charge Circuit

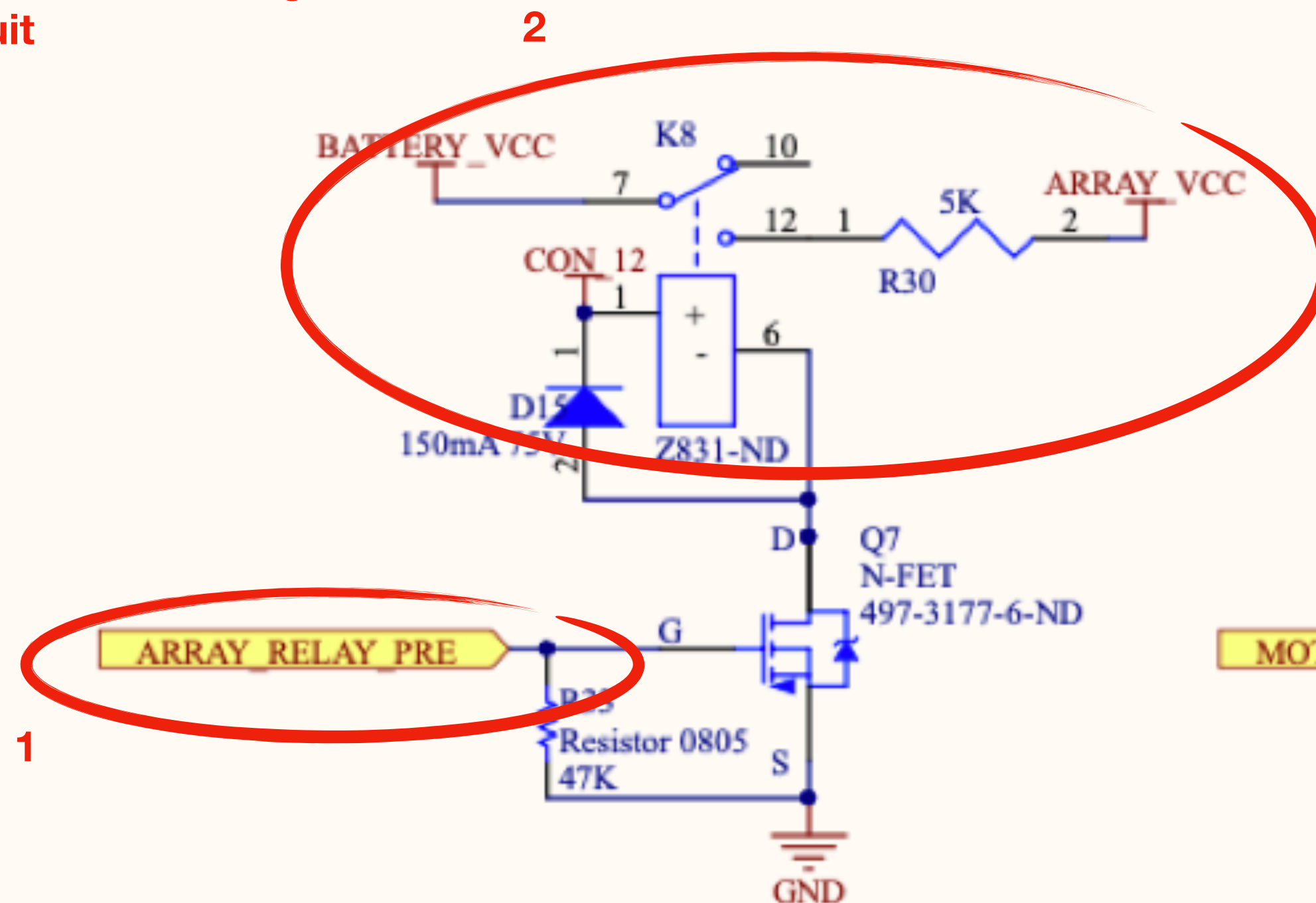

If pre-charge doesn't work, that can cause large start-up currents.

1 → pre-charge isn't getting a signal from the microcontroller or the pre-charge TIME is too short


2 → pre-charge IS getting a signal but for some reason isn't turning on... or isn't pre-charging the circuit

This is the contractor, if it failed in the ON position we could be reading high startup currents since the system would be bypassing the pre-charge circuit!

1 -> something is WRONG with the signal going into the contractor, it's always on or turning on too soon?

2 -> something is wrong with the contractor itself, either it failed open or something else is weird

Can something be wrong with this?

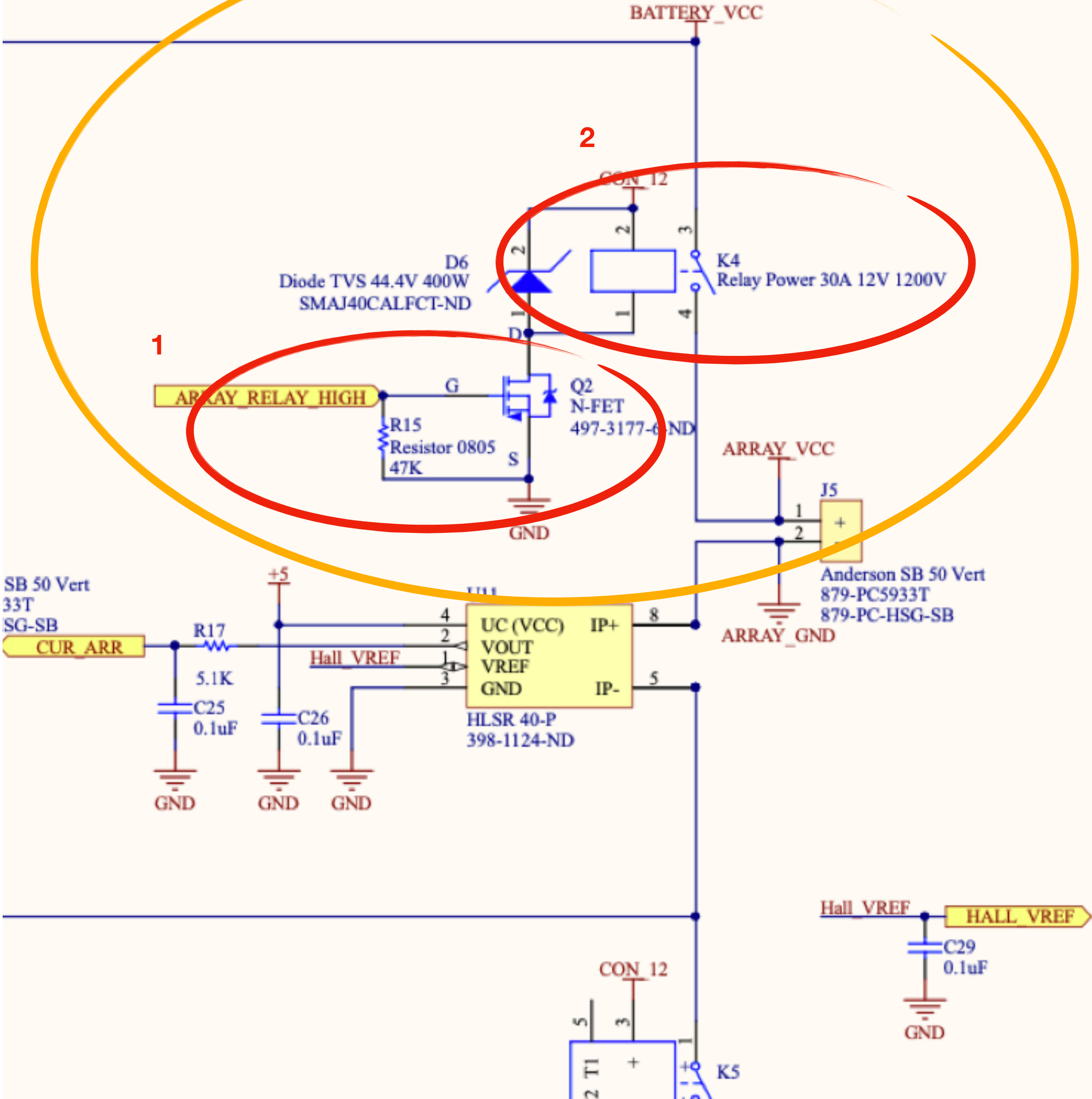


This is the Current sensor, it's suspicious because that's where we get the current readings from.

1 → all the signals are correct but for some reason it's being READ incorrectly or being disrupted by the time it gets to the MC

2 → something is wrong with the CURRENT sensor, it's blown or faulty or something

3 → there's interference with the contractor and the current sensor when the contractor turns on because contractors produce a magnetic field

Can something be wrong with this?

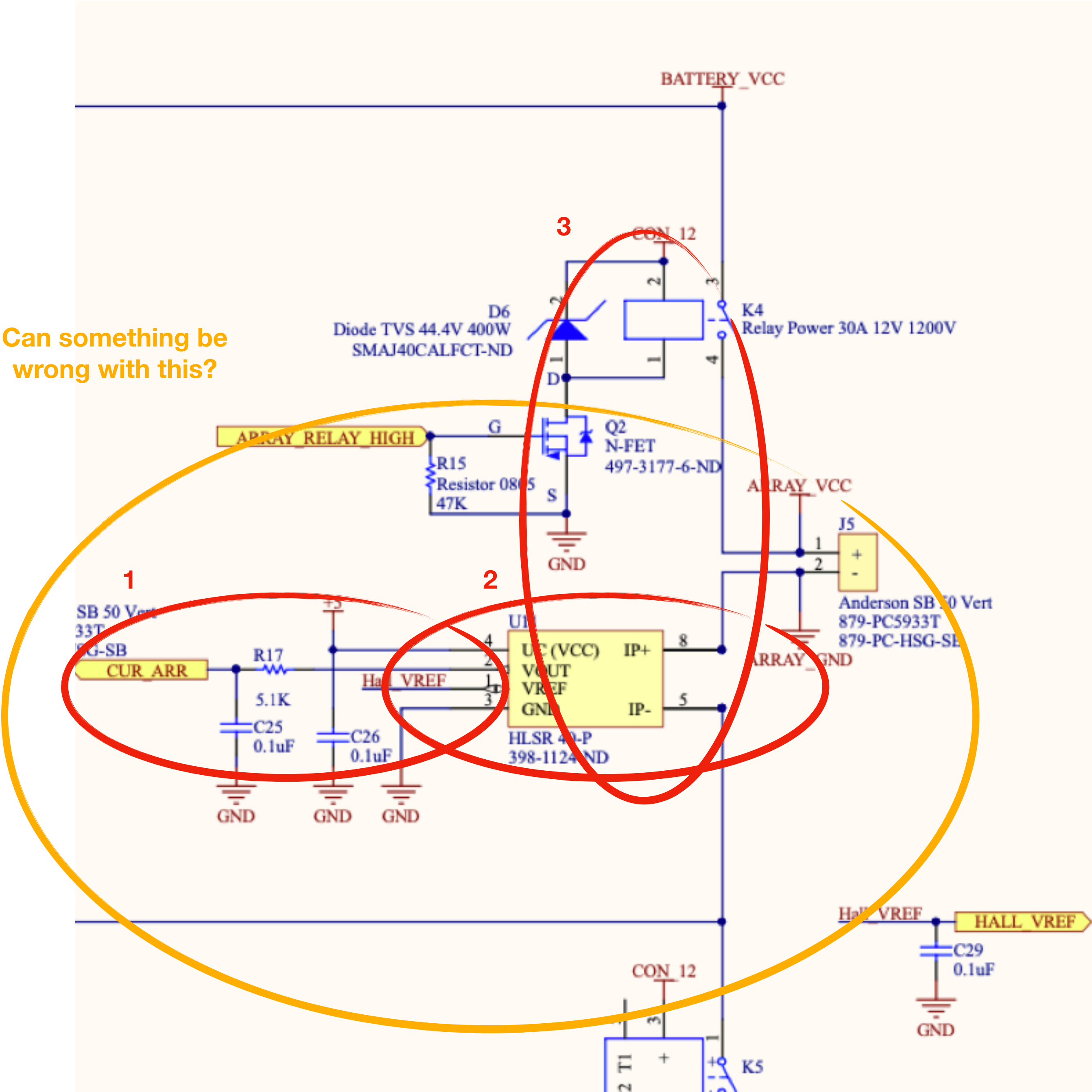


Ok what are we MOST
SUSpicious of?



Ok what are we MOST SUSpicious of?




(Or what's the easiest
thing to check?)

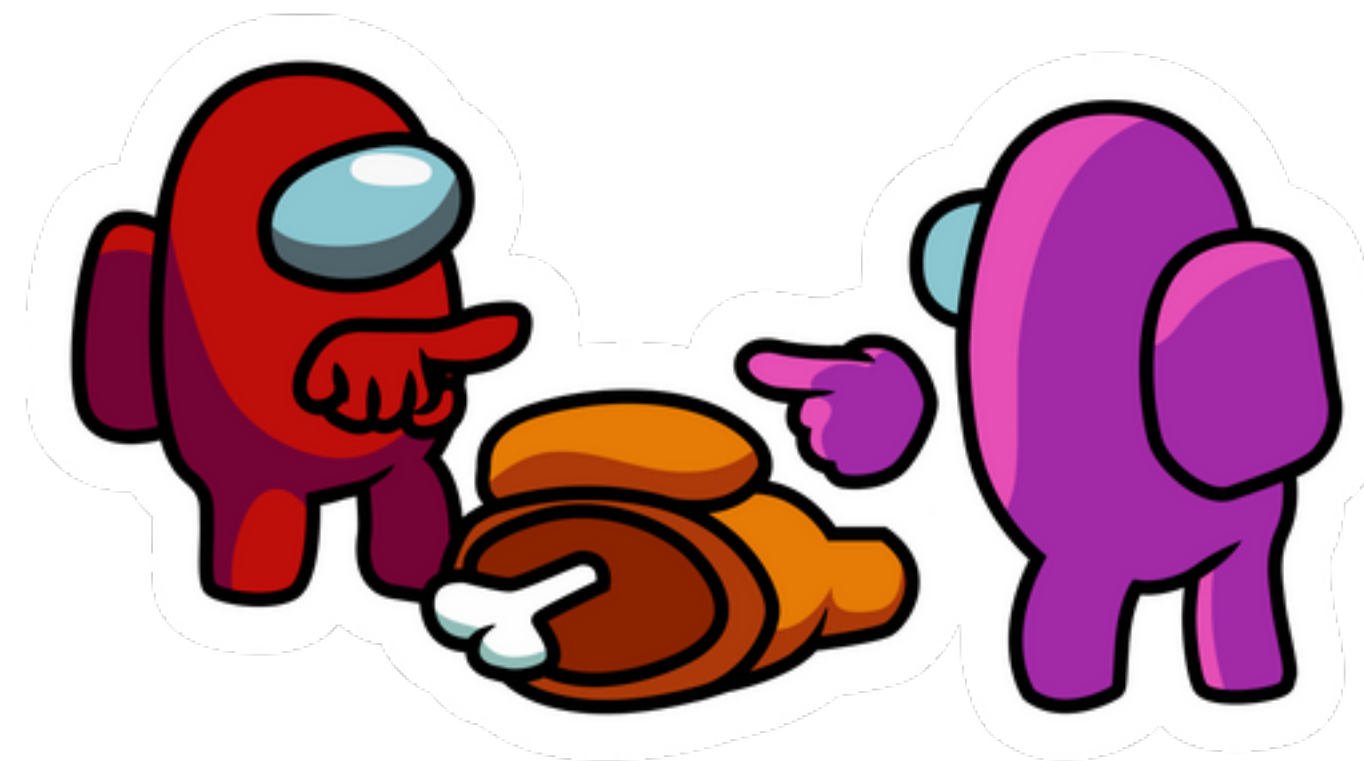



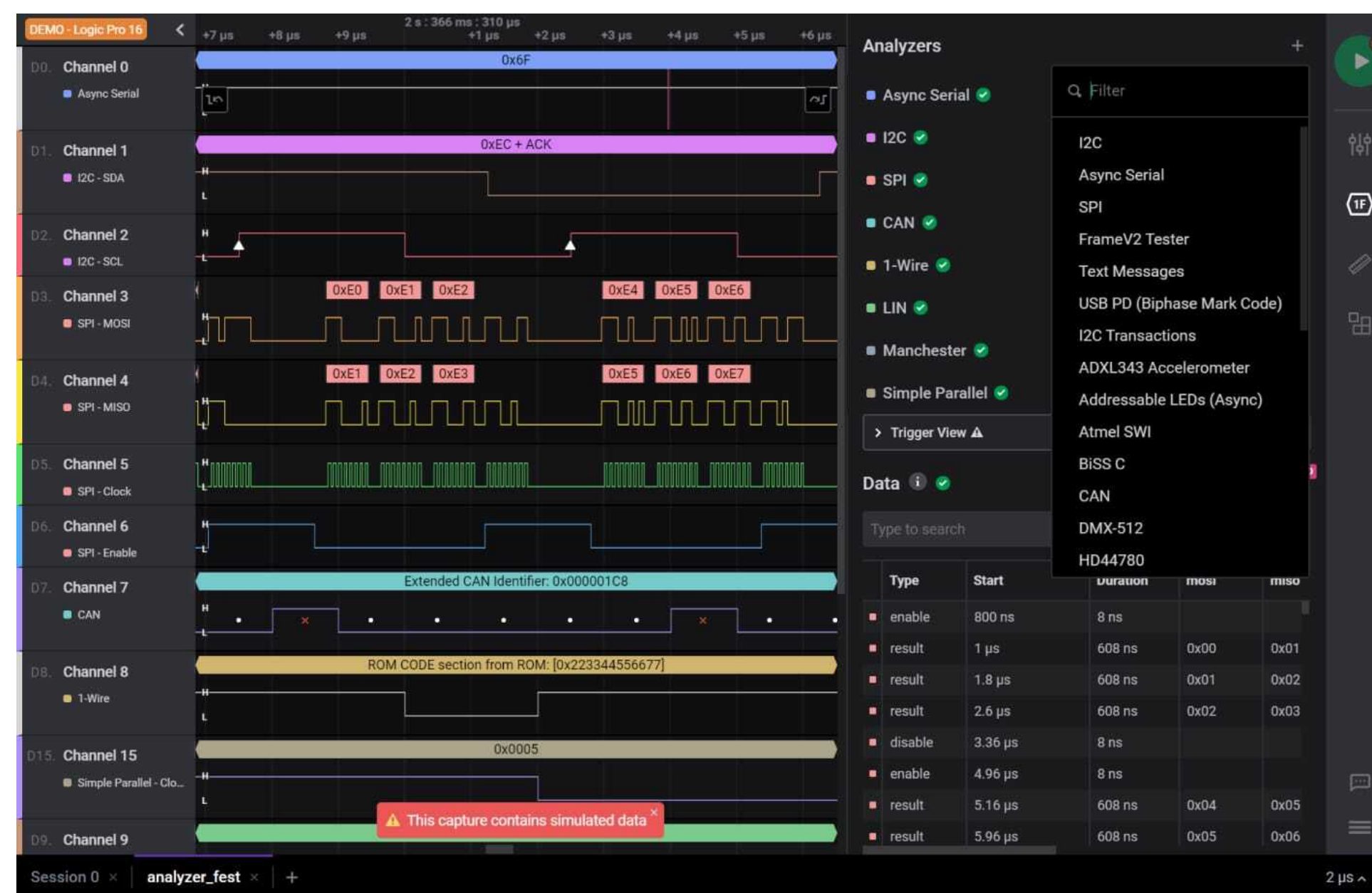Scope → analog
Logic Analyzer → digital
+ communications



Your turn, what would you probe?

You tell me, I'll give you info, and let's see if we can solve the problem.


In summary...

The pre-charge relay blew which caused high inrush current. So no pre-charge, so overcurrent error.

The high inrush current welded the contacts of the contractor together. So the problem persisted when the motor was turned on, because the array was **ALWAYS** on!

TIPS for deBUGging

(Especially during initial bring-up)

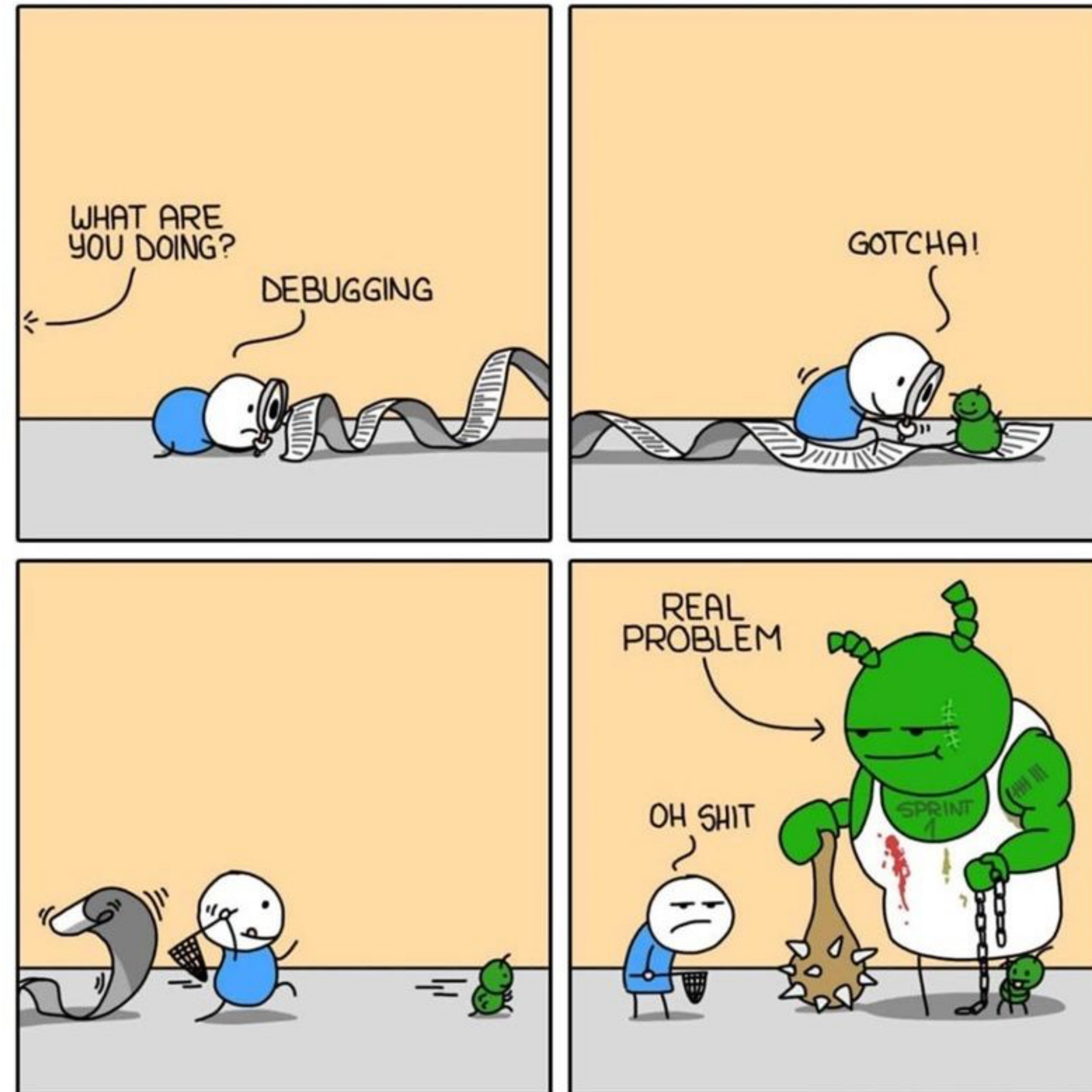

**‘Bring-up’ is the stage
where we slowly +
methodically put together
+ test electrical hardware.**

**‘Bring-up’ is the stage
where we slowly +
methodically put together
+ test electrical hardware.**

**1 - don't assume things are connected
(continuity check everything)**

**‘Bring-up’ is the stage
where we slowly +
methodically put together
+ test electrical hardware.**

- 1 - don't assume things are connected
(continuity check everything)**
- 2 - don't assume things that worked
“yesterday” work “today”**

**‘Bring-up’ is the stage
where we slowly +
methodically put together
+ test electrical hardware.**

1 - don't assume things are connected (continuity check everything)

2 - don't assume things that worked “yesterday” work “today.”

3 - always double check everything is powered, check your voltages, check your signals - sanity check the easy things to get them out of the way so you can find the hard things

**‘Bring-up’ is the stage
where we slowly +
methodically put together
+ test electrical hardware.**

**1 - don't assume things are connected (continuity check
everything)**

**2 - don't assume things that worked “yesterday” work
“today.”**

**3 - always double check everything is powered, check your
voltages, check your signals - sanity check the easy things
to get them out of the way so you can find the hard things**

**4- USE YOUR EXPERIENCE, ONCE A PROBLEM, ALWAYS
A PROBLEM!!!!**

Be. Safe. Be Slow. Be Careful.

**Don't voltage test a battery on current mode
using a multimeter.**

This has been empirically tested.

By me.

GET HELP!

miters.mit.edu

pcb.mit.edu

Your friends!!! Lab staff!! Ppl you know!

Learn from those around you <3

Final tips.

Debugging requires PATIENCE + PRACTICE, there's NO SHORTCUT, even if it can be very frustrating

Think of it this way, every time you debug something, it's an opportunity to LEARN SOMETHING NEW

And learning, is a truly beautiful thing <3